



## Electrical and Electronics Circuits (4190.206A 002)

- HW #1 is due today 3:15pm
- There will be no class on 10/9 (Wed) Hangul Day and new make-up class will be scheduled later.
- The late homework will be accepted only until 10/10 (Thu) 10am. The late submitted homework will receive only 80% of the full credit.




- Self-attendance check




# Review I

## Full Characteristics of MOSFET Device

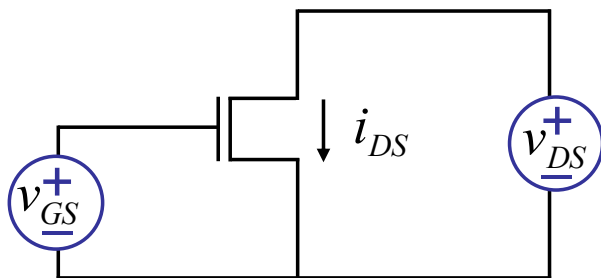

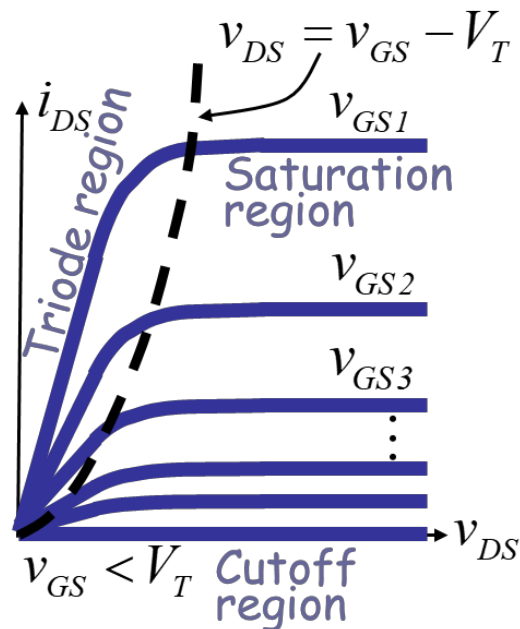
$$i_{DS} = \begin{cases} K \left[ (v_{GS} - V_T)v_{DS} - \frac{v_{DS}^2}{2} \right] & \text{for } v_{GS} \geq V_T \text{ and } v_{DS} < v_{GS} - V_T \\ \frac{K(v_{GS} - V_T)^2}{2} & \text{for } v_{GS} \geq V_T \text{ and } v_{DS} \geq v_{GS} - V_T \\ 0 & \text{for } v_{GS} < V_T \end{cases}$$



- Saturation region → voltage-controlled current source
  - Control voltage:  $v_{GS}$
  - In ideal situation,  $v_{DS}$  should NOT influence any current

$$\frac{K}{2} (v_{GS} - V_T)^2 - \frac{K}{2} (v_{DS} - (v_{GS} - V_T))^2$$

# Review II: Large Signal Analysis

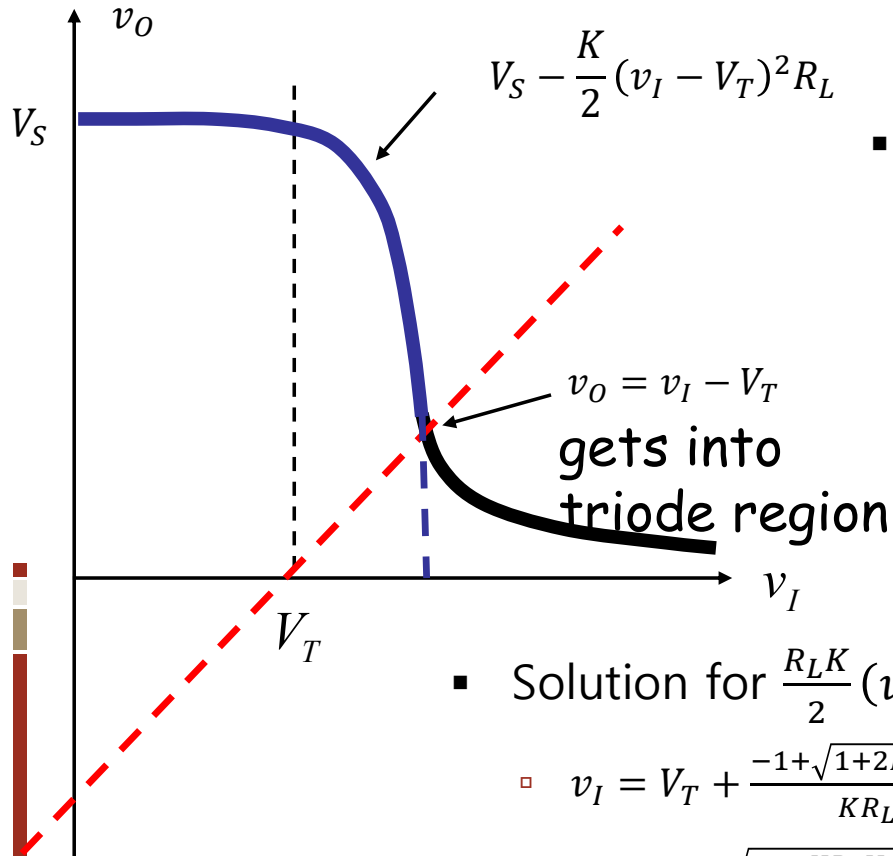

- Where the two curves meet

- $$v_O = V_S - \frac{K}{2}(v_I - V_T)^2 R_L$$
- $$v_O = v_I - V_T$$
- $$\Rightarrow V_S - \frac{K}{2}(v_I - V_T)^2 R_L = (v_I - V_T)$$

- Solution for  $\frac{R_L K}{2}(v_I - V_T)^2 R_L + (v_I - V_T) - V_S = 0$ 
  - $$v_I = V_T + \frac{-1 + \sqrt{1 + 2KR_L V_S}}{KR_L}$$
  - $$v_O = \frac{-1 + \sqrt{1 + 2KR_L V_S}}{KR_L}$$

## Alternative Graphical Method

- Constraint for saturation region

$$i_{DS} = \frac{K}{2}(v_I - V_T)^2 ,$$

for  $v_O \geq v_I - V_T$   
 $\Downarrow$


$$v_O \geq \sqrt{\frac{2i_{DS}}{K}}$$

$\Downarrow$

$$i_{DS} \leq \frac{K}{2}v_O^2$$


- Load relation
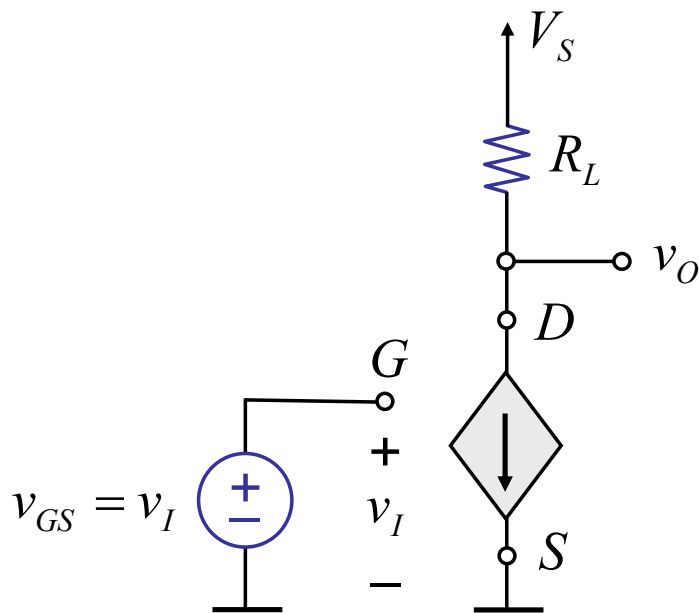
$$i_{DS} = \frac{V_S}{R_L} - \frac{v_O}{R_L}$$


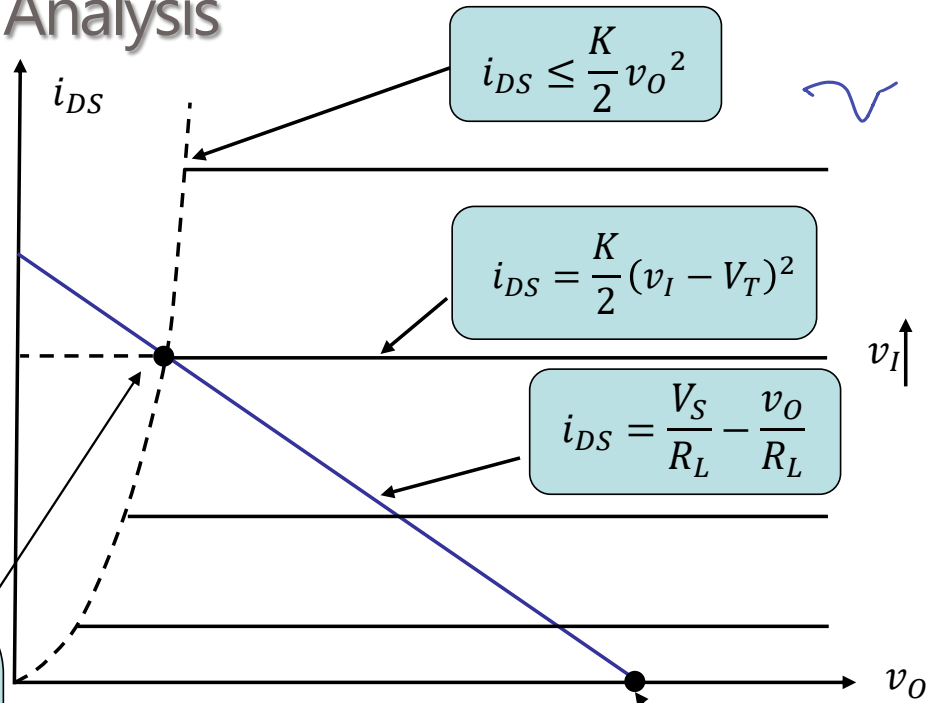
# Alternative Graphical Analysis

- Only interested in the saturation region
- What are the required ranges for  $v_I, v_O, i_{DS}$ ?



$$v_O = \frac{-1 + \sqrt{1 + 2KR_L V_S}}{KR_L}$$


$$v_I = V_T + \frac{-1 + \sqrt{1 + 2KR_L V_S}}{KR_L}$$

$$i_{DS} = \frac{V_S}{R_L} - \frac{v_O}{R_L}$$


$v_I = V_T$  threshold  
 $i_{DS} = 0$  and  $v_O = V_S$
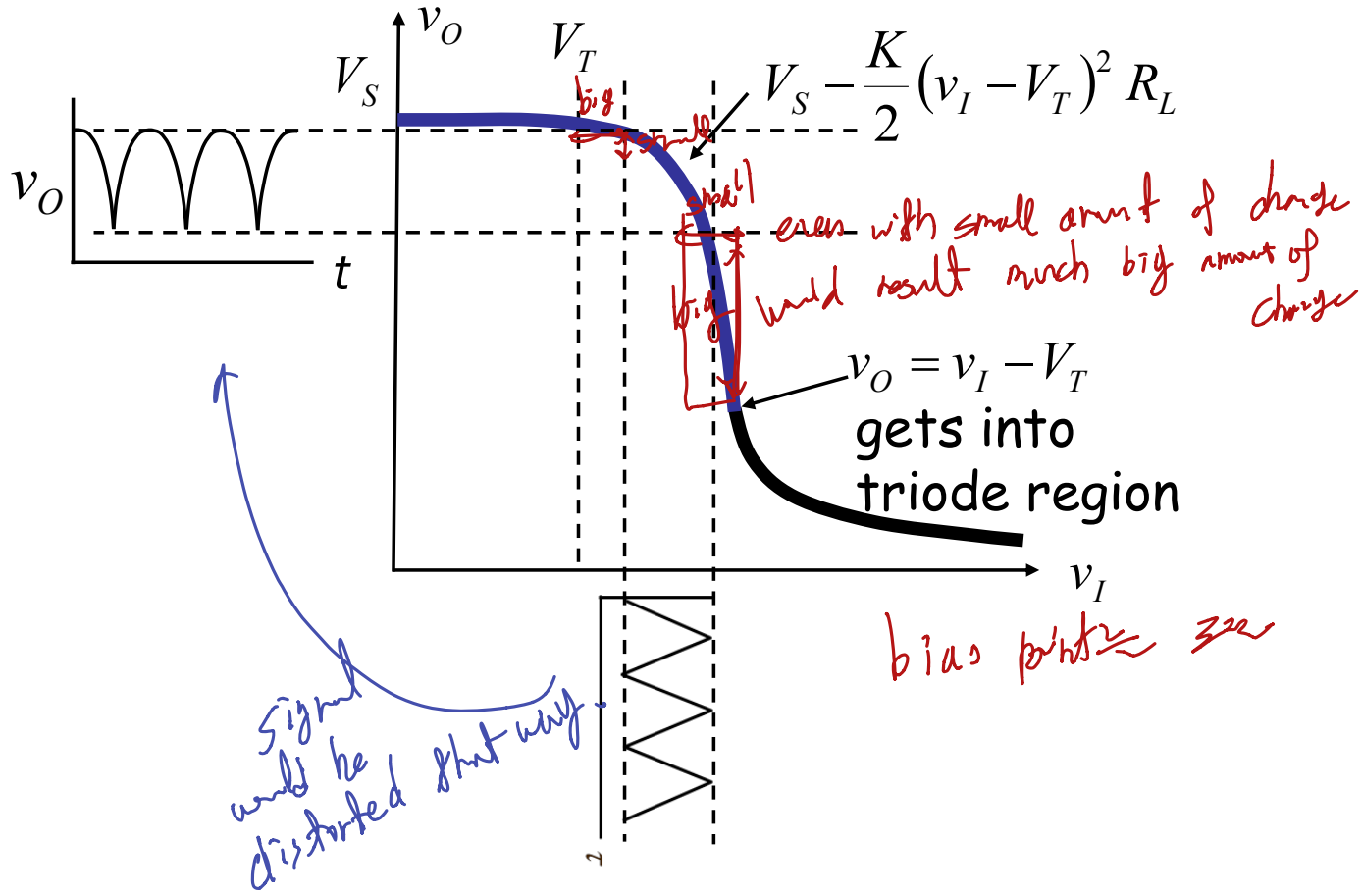
# Large Signal Analysis

- Piecewise analysis for  $v_O$  vs  $v_I$



# Ch. 8 Small Signal Model

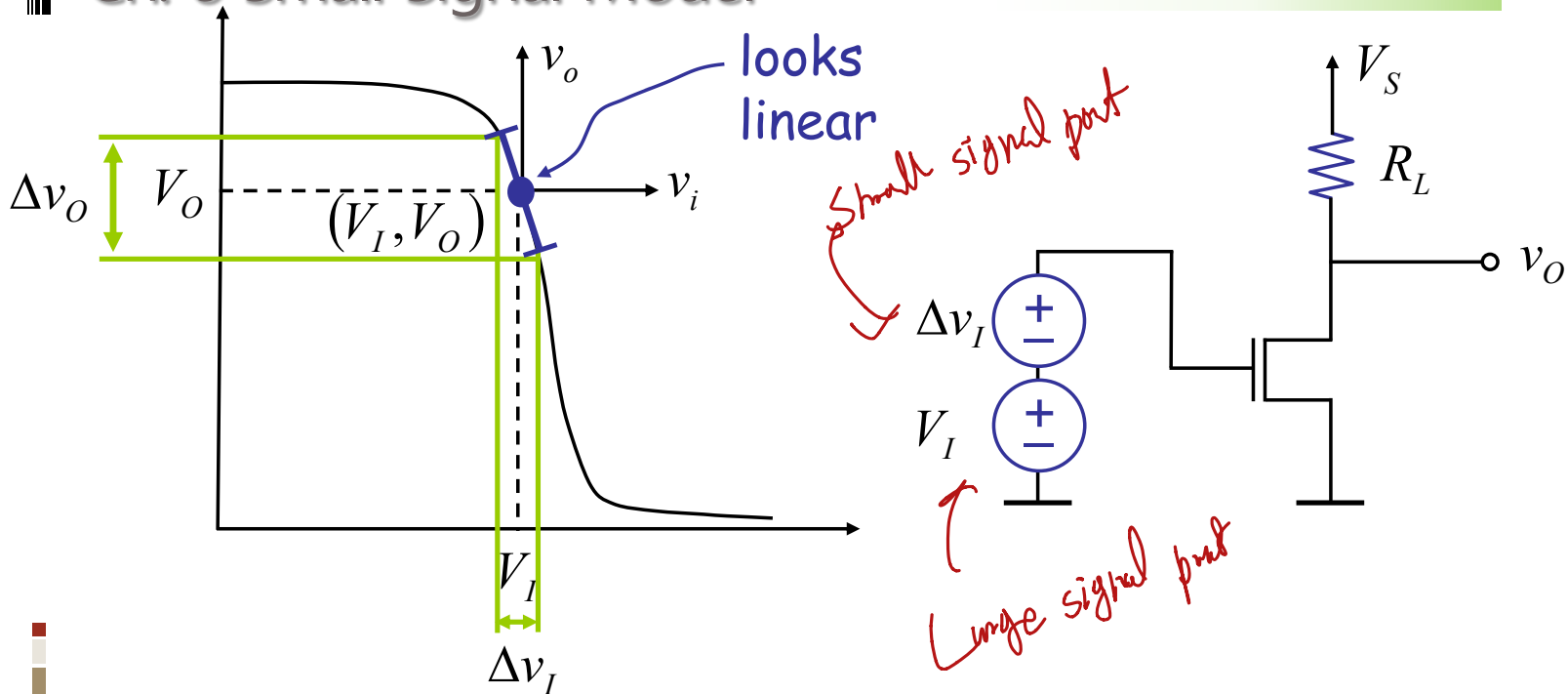

- Operate amp at  $V_I, V_O \rightarrow$  DC bias
- Superimpose small signal on top of  $V_I$
- Notation:  $v_I = V_I + v_i, v_O = V_O + v_o$

## Small Signal Analysis

$$v_o = V_s - \frac{R_L K}{2} (v_I - V_T)^2 \quad \Bigg| \quad V_o = V_s - \frac{R_L K}{2} (V_I - V_T)^2$$

substituting  $v_I = V_I + \underbrace{v_i}_{v_i \ll V_I}$

$$v_o = V_s - \frac{R_L K}{2} ([V_I + v_i] - v_T)^2$$

$$= V_s - \frac{R_L K}{2} ([V_I - V_T] + v_i)^2$$

$$= V_s - \frac{R_L K}{2} ([V_I - V_T]^2 + 2[V_I - v_T]v_i + \cancel{v_i^2})$$

$$V_o + v_o = V_s - \frac{R_L K}{2} (V_I - V_T)^2 - R_L K (V_I - V_T) v_i$$


$$v_o = -R_L K \underbrace{(V_I - V_T)}_{g_m \text{ related to } V_I} v_i$$

➔ Same result can be also obtained by differentiation.





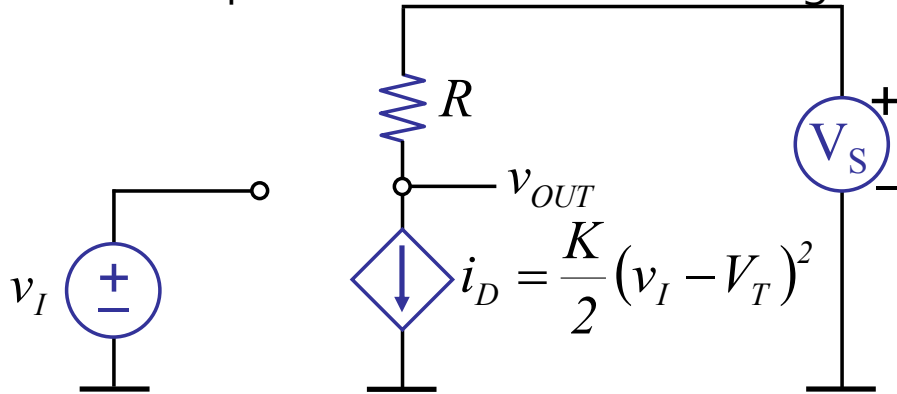
# Small Signal Circuit

- We can derive equivalent models for small signal circuit



Large signal

Small signal

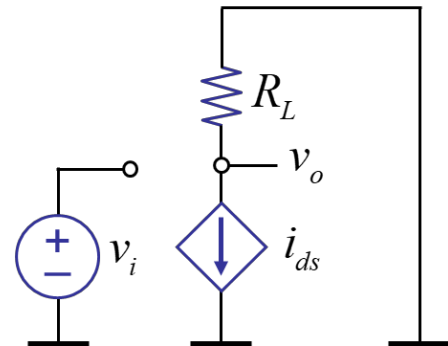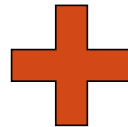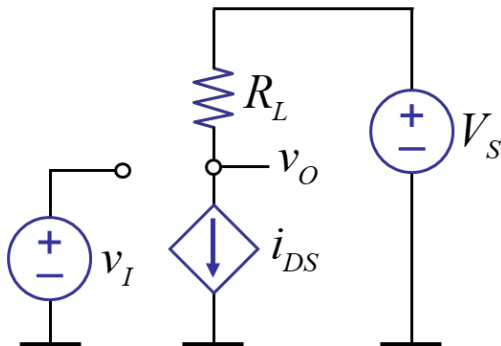

# Small Signal Circuit

- To find the relationship between the small signal parameters of a circuit, we can replace large signal device models with corresponding small signal device models, and then analyze the resulting small signal circuit.

- KVL, KCL applied to some circuit C yields:

$$\dots + V_A + \dots + V_{OUT} + \dots + V_B + \dots$$

~~1~~ top half of the circuit

- Replace total variables with operating point variables plus small signal variables

$$\dots + V_A + V_a \dots + V_{OUT} + V_{out} \dots + V_B + V_b + \dots$$

- Operating point variables themselves satisfy the same KVL, KCL equations

$$\dots + V_A \dots + V_{OUT} \dots + V_B + \dots$$

bias point only.

- So, we can cancel them out, leaving

$$\dots + V_a \dots + V_{out} \dots + V_b + \dots$$

2 final results: changes for the same

- But 2 is the same equation as 1 with small signal variables replacing total variables, so 2 must reflect same topology as in C, except that small signal models are used.


- Since small signal models are linear, our linear tools will now apply...

# Small Signal Circuit Analysis

1. Find operating point using DC bias inputs using large signal model.
2. Develop small signal (linearized) models for elements.
3. Replace original elements with small signal models.

Once small signal circuit with only linearized elements is obtained, we can use all the linear circuit analysis tools such as superposition and Thevenin equivalent circuits.

# Small Signal Model of MOSFET

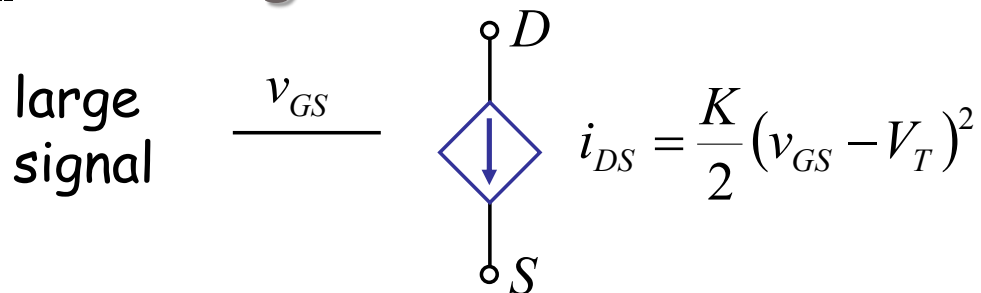


Small signal analysis:

$$i_{DS} = \frac{K}{2} (v_{GS} - V_T)^2$$

$$i_{ds} = \frac{\partial}{\partial v_{GS}} \left[ \frac{K}{2} (v_{GS} - V_T)^2 \right] \bigg|_{v_{GS}=V_{GS}} \cdot v_{gs}$$

$$i_{ds} = \underbrace{K(V_{GS} - V_T)}_{g_m} \cdot v_{gs}$$

small  
signal  
model

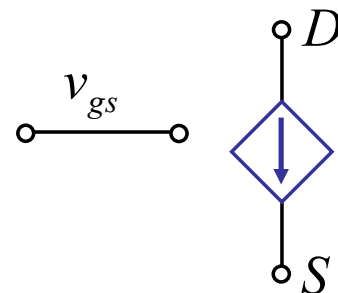

$$i_{ds} = K(V_{GS} - V_T) v_{gs}$$


$$i_{ds} = g_m v_{gs}$$




$i_{ds}$  is linear in  $v_{gs}$

# Small Signal Model of DC Voltage Source

large  
signal

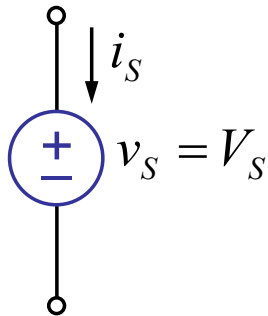


small  
signal  
model

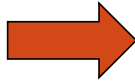

Small signal


$$v_s = \left. \frac{\partial V_S}{\partial i_S} \right|_{i_S = I_S} \cdot i_s$$

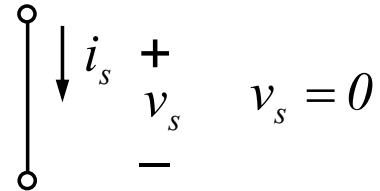


DC voltage source behaves  
as short to small signals.

# Small Signal Model of DC Current Source

large  
signal

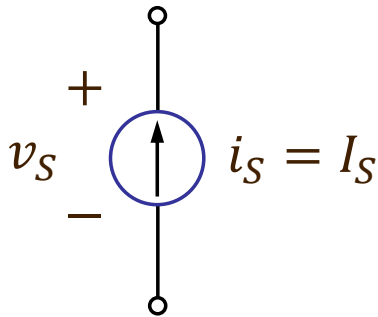


small  
signal  
model

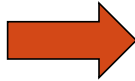

Small signal


$$i_s = \left. \frac{\partial I_S}{\partial v_S} \right|_{v_S = V_S} \cdot v_s$$

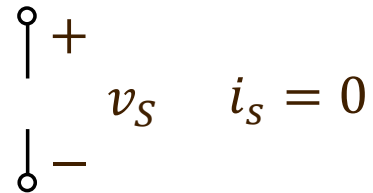

DC current source behaves  
as open circuit to small  
signals.

# Small Signal Model of Resistor

Large signal

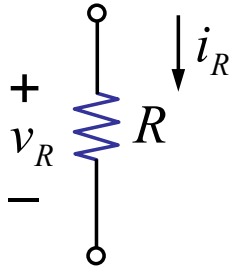



Small signal analysis:

$$v_R = R i_R$$

$$v_r = \left. \frac{\partial(R i_R)}{\partial i_R} \right|_{i_R = I_R} \cdot i_r$$

$$v_r = R \cdot i_r$$

small  
signal  
model

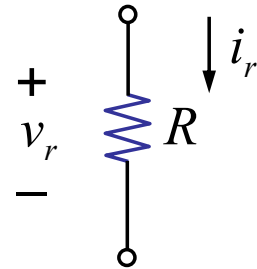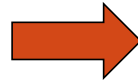




# Large Signal and Small Signal Circuits

↓  $v_{gs} > V_{th}$ ? (No)  
→ to get this.

## Large signal

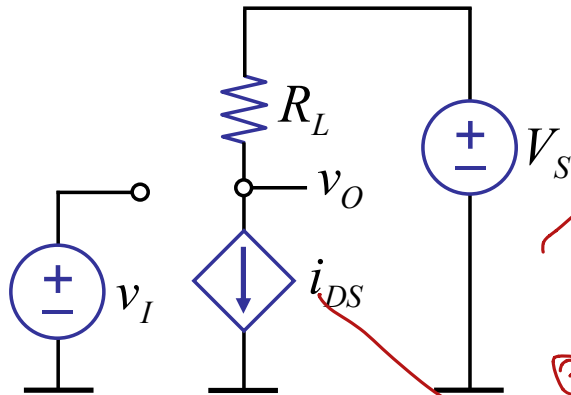


Linearize

② analyze is needed

$$i_{DS} = \frac{K}{2} (v_I - V_T)^2$$

$$v_O = V_S - \frac{K}{2} (v_I - V_T)^2 R_L$$

## Small signal

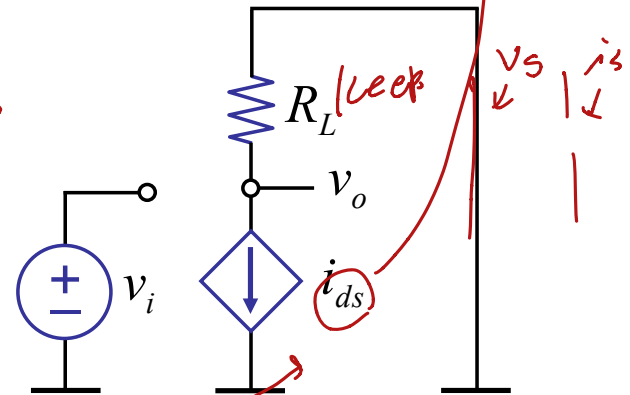

$$i_{ds} = K(V_I - V_T) \cdot v_i$$

$$i_{ds} R_L + v_o = 0$$

$$v_o = -i_{ds} R_L$$

$$v_o = -K(V_I - V_T) R_L \cdot v_i$$

$$= -g_m R_L \cdot v_i$$

- To obtain this value, we need a bias value. Therefore large signal should be done before small signal analysis.