



## Electrical and Electronics Circuits (4190.206A 002)

- HW #2 is out and due on Oct. 23, 3:15pm
- 1<sup>st</sup> mid-term exam will be in the next week. I will finalize the date by the next class.




- Self-attendance check



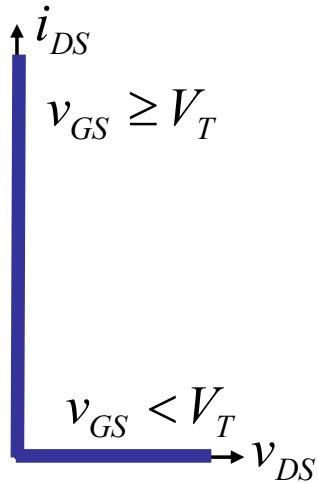
# Review I

- MOSFET (Metal-Oxide-Semiconductor Field-Effect Transistor)




S MODEL

for quick  
digital analysis

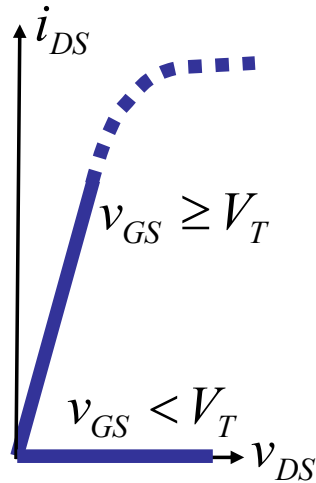

SR MODEL

for digital  
designs


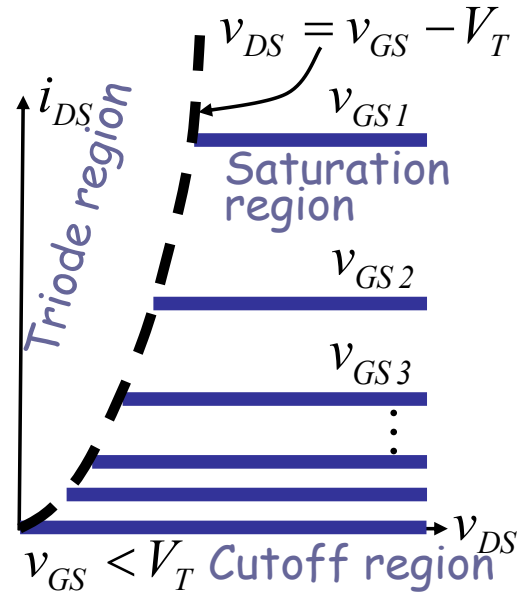


SCS MODEL


for analog  
designs

# Review II

- Typical configuration for amplifier

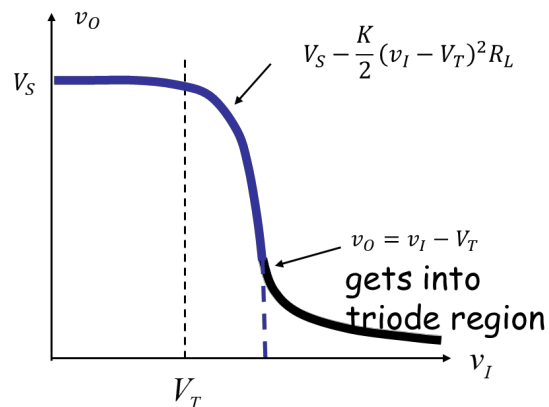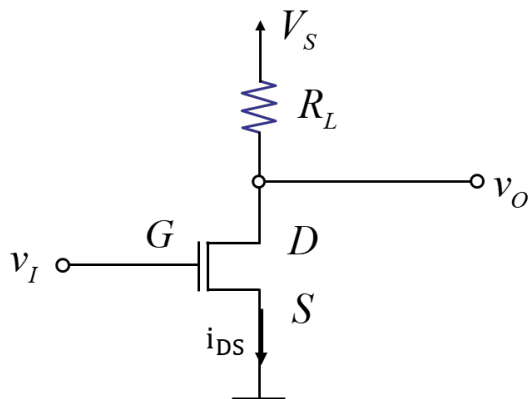


- Small signal model



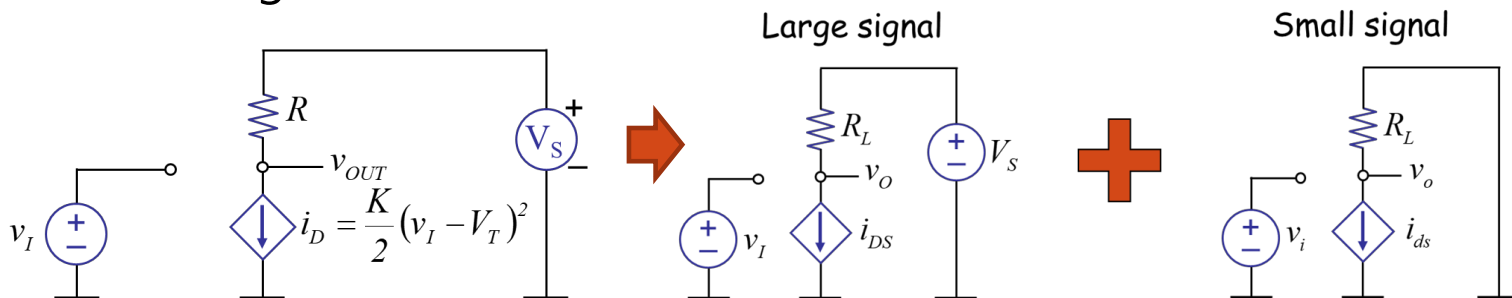

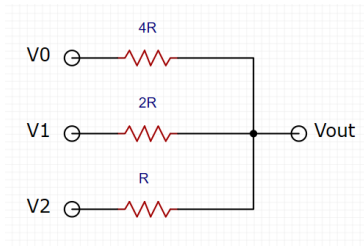
# Connecting Two Circuits

- What happens if we connect a load to the output of DAC?



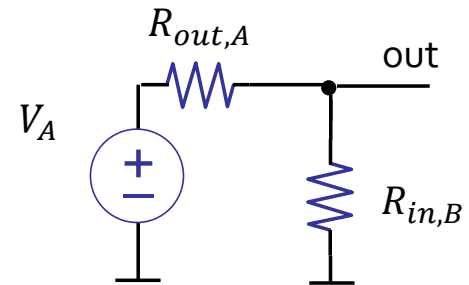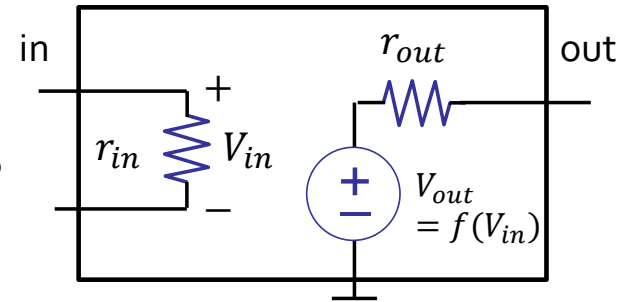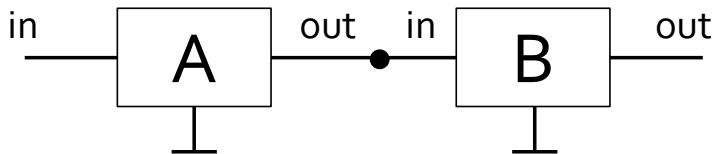- Design rule of thumb
  - Assume that circuit A drives circuit B
  - $R_{out,A}$ : output resistance of circuit A
  - $R_{in,B}$ : input resistance of circuit B
  - Make sure that  $R_{out,A} \leq R_{in,B}$







## Where we are...

- Chap. 9 Energy Storage Elements
  - 9.1 Constitutive Laws
    - 9.1.1 Capacitors
    - 9.1.2 Inductors
  - 9.2 Series and Parallel Connections
  - 9.3 Special Examples
  - 9.5 Energy, Charge, and Flux Conservation
- Chap. 10 First-order Transients in Linear Electrical Networks
  - 10.1 Analysis of RC Circuits
  - 10.2 Analysis of RL Circuits
  - 10.4 Propagation Delay and the Digital Abstraction
  - 10.7 Digital Memory









# Motivation

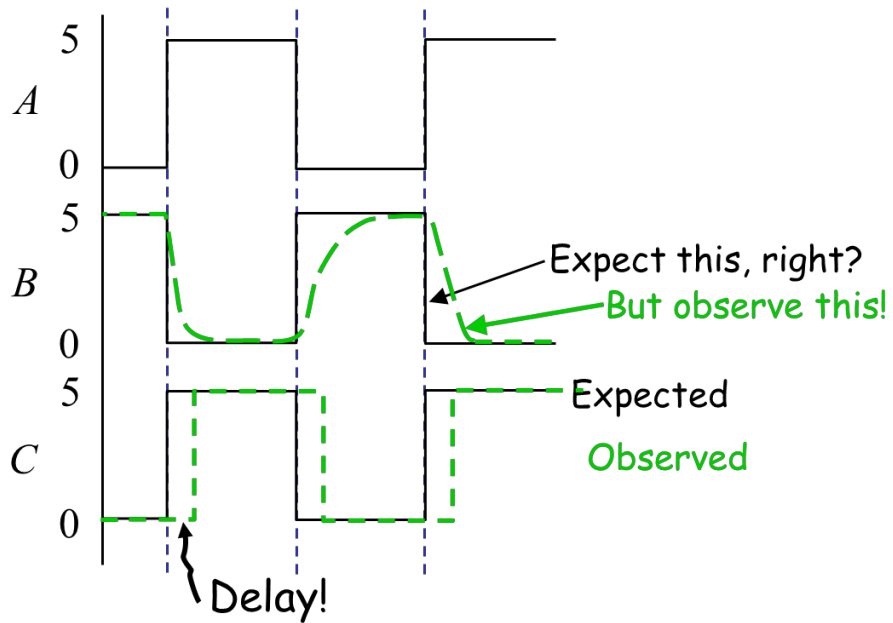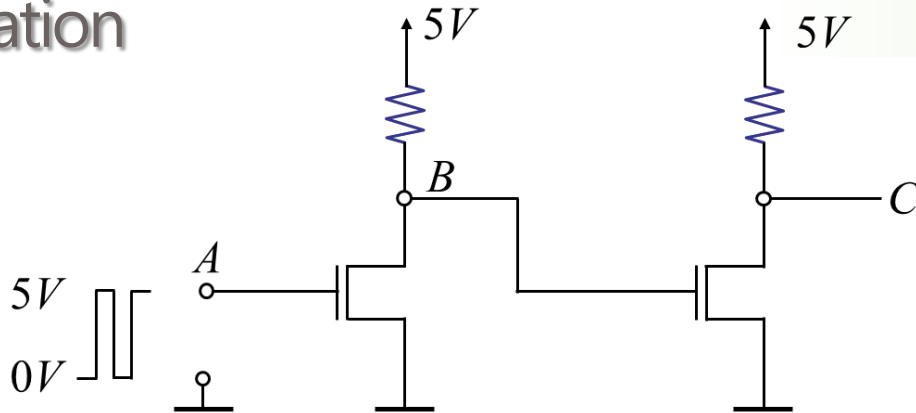


# Capacitance in MOSFET

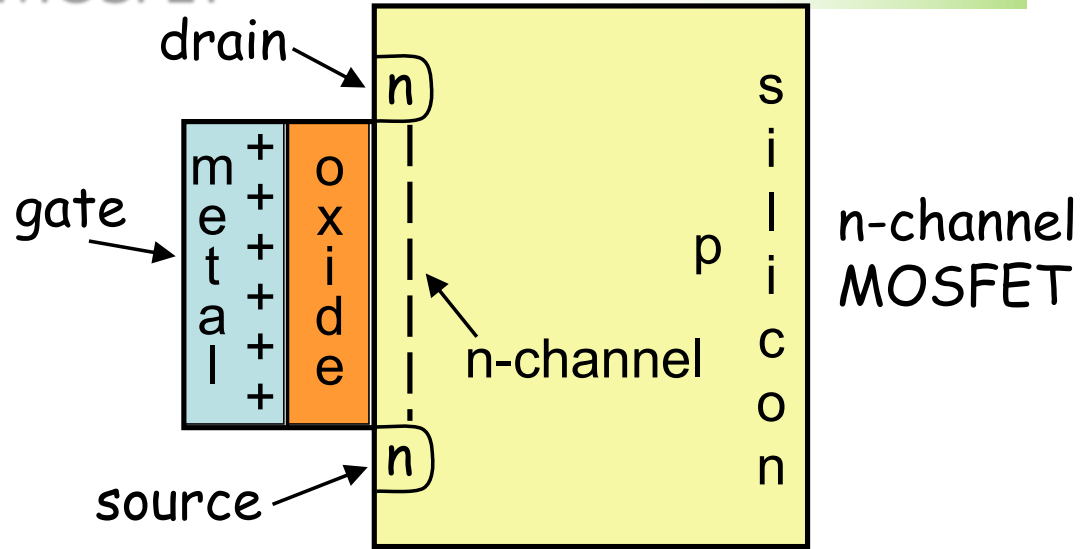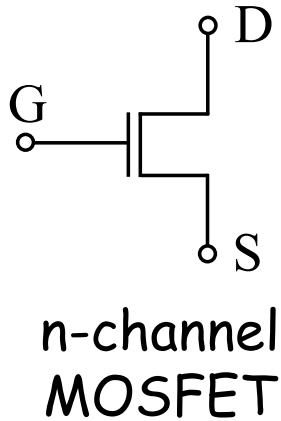


Realistic  
MOSFET

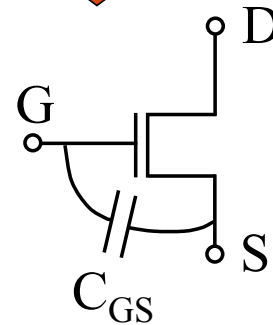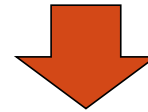

# Ideal Linear Capacitor

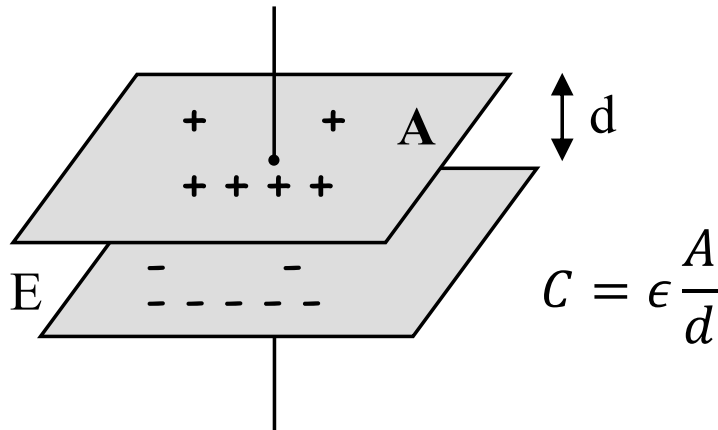

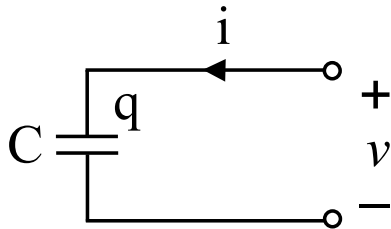obeys Lumped  
Matter Discipline!  
total charge on  
capacitor  
 $= +q - q = 0$




$$q = C v$$

coulombs      farads      volts





# Ideal Linear Capacitor

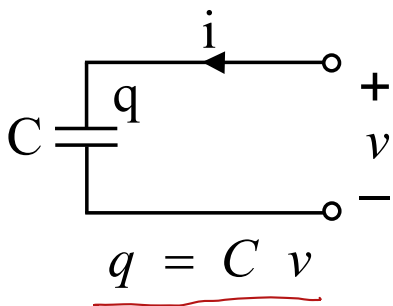


$$\begin{aligned} i &= \frac{dq}{dt} \\ &= \frac{d(Cv)}{dt} \\ &= C \frac{dv}{dt} \end{aligned}$$

$$\frac{d\omega_E(t)}{dt} = i(t)v(t)$$


$$d\omega_E(t) = v(t)(i(t)dt) = v(t)dq(t)$$
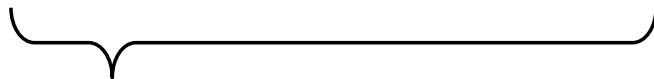
$$\omega_E = \int_0^q v dx = \frac{q^2(t)}{2C} = \frac{Cv(t)^2}{2}$$




A capacitor is an energy storage device  
→ memory device → history matters!


# Current Source and Capacitor

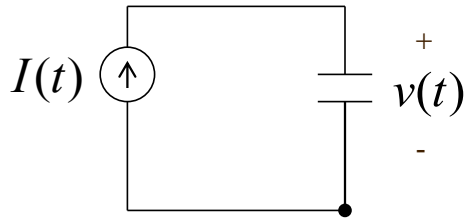

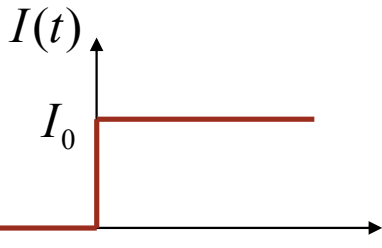
What is the voltage across the capacitor?



Step input

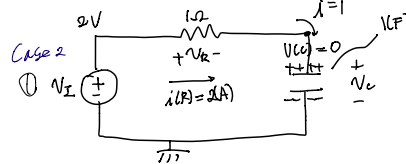


Case 1.)  $Q = 0(C)$   $V_S = 0(V)$   
 $V_C = 0(V)$   $V_R = 0, i_R = 0$



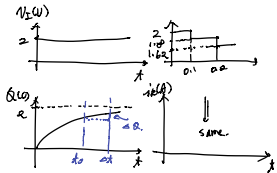


Case 2.)  $Q = 0(C)$   $V_S = 2(V)$   
 $V_C = 0$   $V_R = 2V, i_R = 2A$   
 $\Delta Q = \frac{V_S - V_C}{R} \cdot \Delta t$

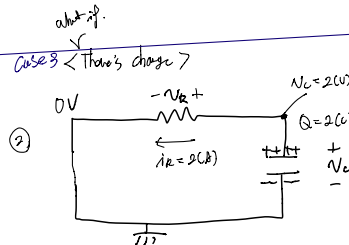
$\lim_{\Delta t \rightarrow 0} C \frac{\Delta V_C}{\Delta t} = \frac{\Delta Q}{\Delta t} = \frac{V_S - V_C}{R} \Rightarrow RC \cdot \frac{dV_C}{dt} = V_S - V_C$



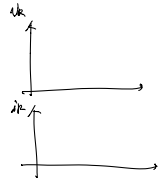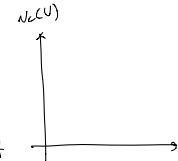
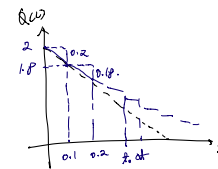
Case 3  $\frac{C \Delta V_C}{\Delta t} = -\frac{N_C - 0}{R} \Rightarrow RC \cdot \frac{dV_C}{dt} + V_C = 0$




# Voltage Source and Capacitor

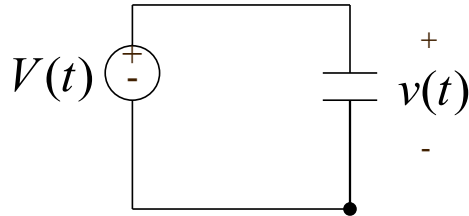

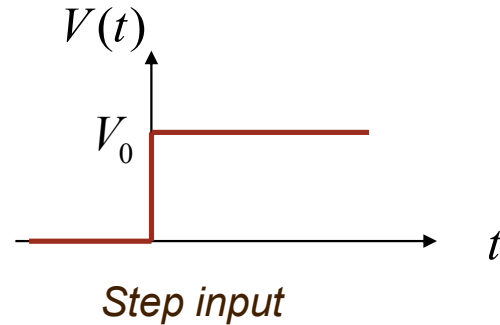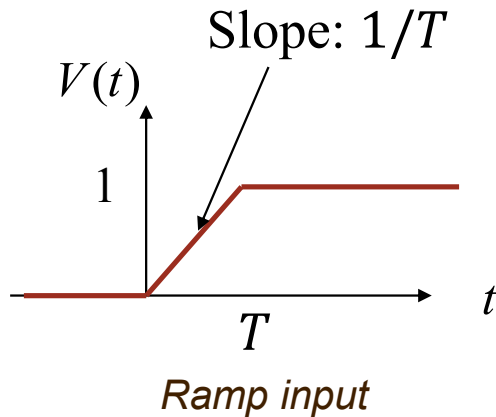What is the current through the capacitor?



# Unit Impulse Function

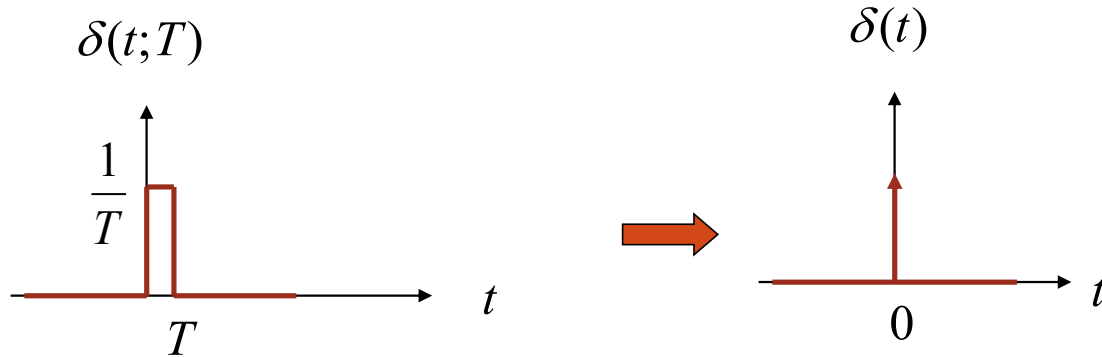


$$\delta(t) = 0 \quad \text{for } t \neq 0$$

$$\int_{-\infty}^t \delta(t) dt = u(t) \Leftrightarrow \delta(t) = \frac{du(t)}{dt}$$

$$\int_{-\infty}^{+\infty} \delta(t) dt = 1$$

## Analysis of an RC circuit (Section 10.1)

## Thévenin Equivalent:

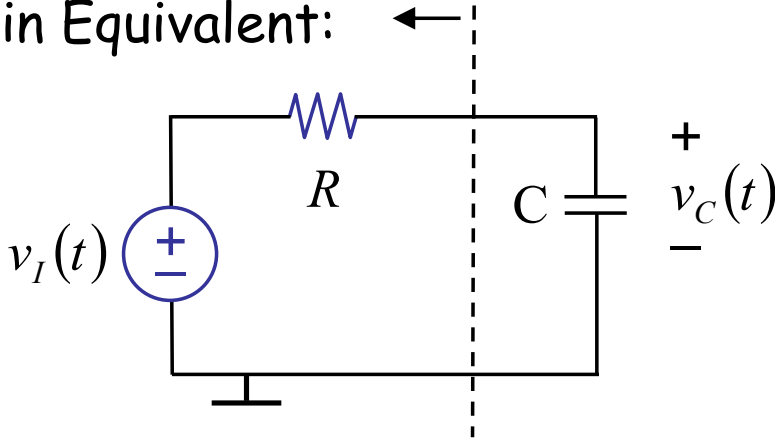

in Case 3)  $P.C. \frac{dN_C}{dt} + V_C = 0$ .

$N_C$  ↑  
Initial change of capacitor  
→  $\frac{dN_C}{dt}$  ↓

should satisfy that condition.  
② ③  
finding value: objective  
just unknown  
①

$\therefore \frac{1}{at} = a^{-t} = e^{-\ln(a)t} = e^{-st} \Rightarrow e^{st}$

$P.C. \frac{dN_C}{dt} + V_C = 0 \Rightarrow \dots \Rightarrow S = -\frac{1}{RC} \Rightarrow$

definite sol.  
 $V_C = e^{-\frac{1}{RC}t}$   
②  
①  
do again registration  
q. No. well defined initial condition so there will be infinite number of equations and sol.


## Node method:

$$\frac{v_C - v_I}{R} + C \frac{dv_C}{dt} = 0$$

$$RC \frac{dv_C}{dt} + v_C = v_I \quad \begin{cases} t \geq t_0 \\ v_C(t_0) \text{ given} \end{cases}$$

RC time constant

## Example Analysis of an RC circuit

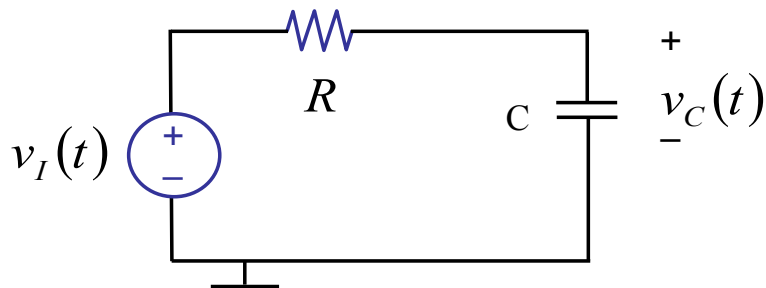

$$v_I(t) = V_I$$

$$v_C(0) = V_0 \quad \text{given}$$

$$RC \frac{dv_C}{dt} + v_C = V_I \quad \text{—————} \otimes$$

## Example Analysis of an RC circuit

$$v_I(t) = V_I$$

$$v_C(0) = V_0 \quad \text{given}$$

$$RC \frac{dv_C}{dt} + v_C = V_I \quad \text{—————} \quad (\otimes)$$

$$v_C(t) = v_{CH}(t) + v_{CP}(t)$$

total    homogeneous    particular

### Method of homogeneous and particular solutions:

1. Find the homogeneous solution.
2. Find the particular solution.
3. The total solution is the sum of the particular and homogeneous solutions.
4. Use the initial conditions to solve for the remaining constants.

# Homogeneous Solution

$$RC \frac{dv_{CH}}{dt} + v_{CH} = 0 \quad \text{---} \quad \textcircled{y}$$

$v_{CH}$ : solution to the homogeneous  $\textcircled{y}$  equation  
(set drive to zero)

$v_{CH} = Ae^{st}$  assume solution of this form.  $A, s$  ?

$$RC \frac{dAe^{st}}{dt} + Ae^{st} = 0 \quad R C A s \cancel{e^{st}} + A \cancel{e^{st}} = 0$$

Discard trivial  $A = 0$  solution,

$$RCs + 1 = 0 \quad \text{Characteristic equation}$$

$$\longrightarrow s = -\frac{1}{RC}$$

$$v_{CH} = Ae^{\frac{-t}{RC}} \quad \text{RC called time constant } \tau$$



## Particular Solution

$$RC \frac{dv_{CP}}{dt} + v_{CP} = V_I$$

$$v_{CP} = V_I \quad \text{works}$$

$$RC \frac{dV_I}{dt} + V_I = V_I$$

0

In general, use trial and error.

$v_{CP}$ : any solution that satisfies the original equation (X)



## Total Solution

$$v_C = v_{CP} + v_{CH}$$

$$v_C = V_I + A e^{\frac{-t}{RC}}$$

Find remaining unknown from initial conditions:

Given,  $v_C = V_0$  at  $t = 0$

so,  $V_0 = V_I + A$

or  $A = V_0 - V_I$


thus 
$$v_C = V_I + (V_0 - V_I) e^{\frac{-t}{RC}}$$

also 
$$i_C = C \frac{dv_C}{dt} = -\frac{(V_0 - V_I)}{R} e^{\frac{-t}{RC}}$$



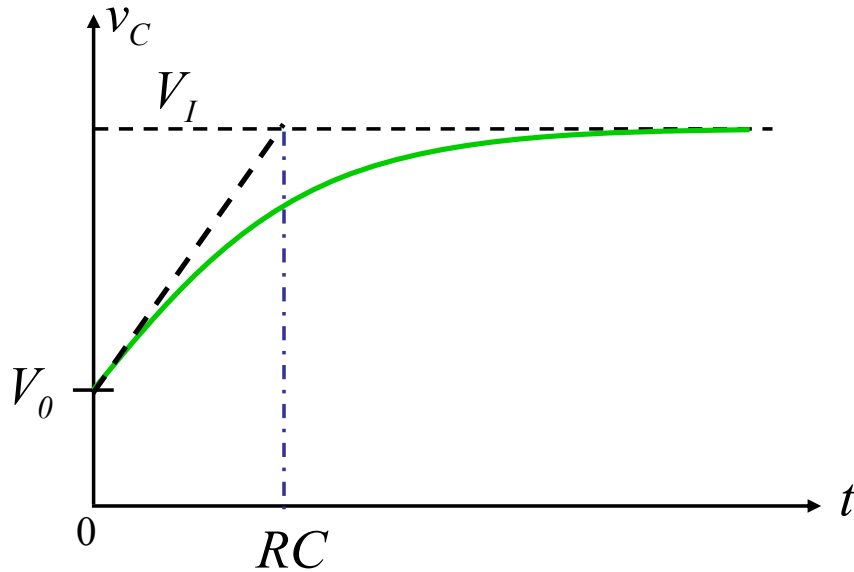
# Plot of Total Solution

$$v_C = V_I + (V_0 - V_I) e^{\frac{-t}{RC}}$$



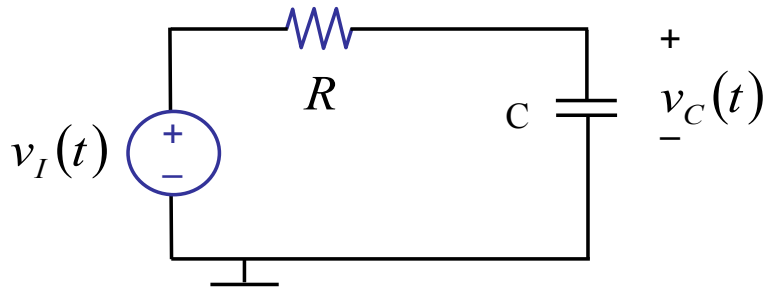
# Intuitive Analysis



- Response to step input
- $v_C = V_I + (V_0 - V_I)e^{-t/RC} = V_I(1 - e^{-t/RC}) + V_0e^{-t/RC}$
- At  $t = 0$ ,  $1 - e^{-\frac{t}{RC}} = 0$  and  $e^{-t/RC} = 1$
- At  $t = \infty$ ,  $1 - e^{-\frac{t}{RC}} = 1$  and  $e^{-t/RC} = 0$
- Especially at  $t = \infty$ , treat capacitor as open circuit



## Double Inverter Circuit


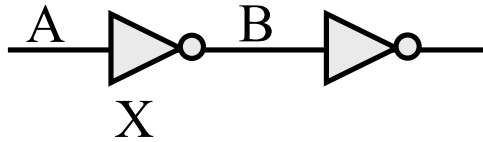


First, rising delay  $t_r$  at B

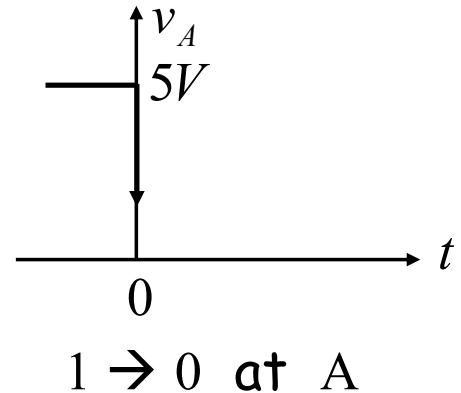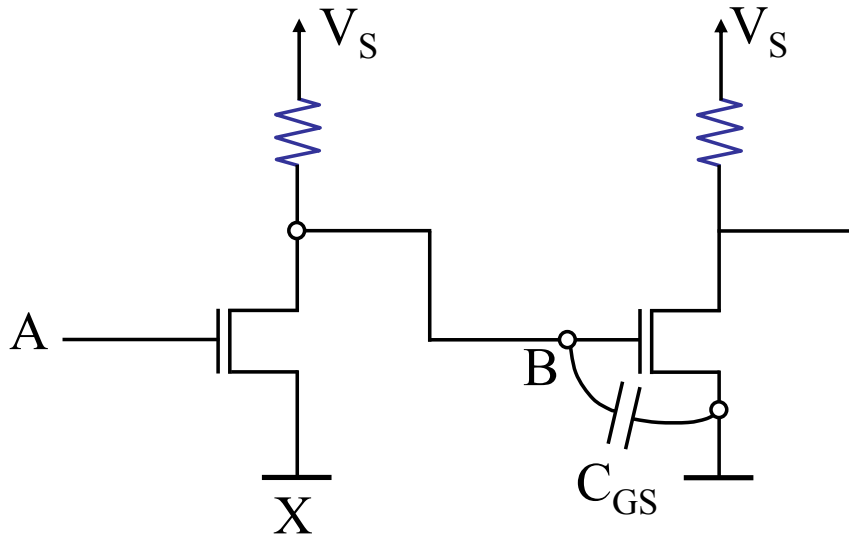


# Double Inverter Circuit

Rising Delay  $t_r$  at B

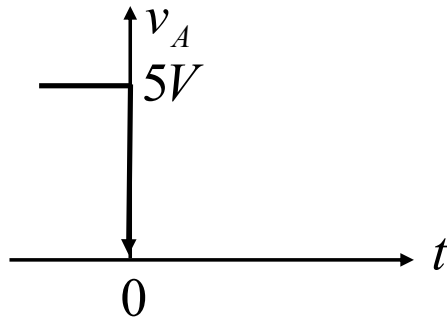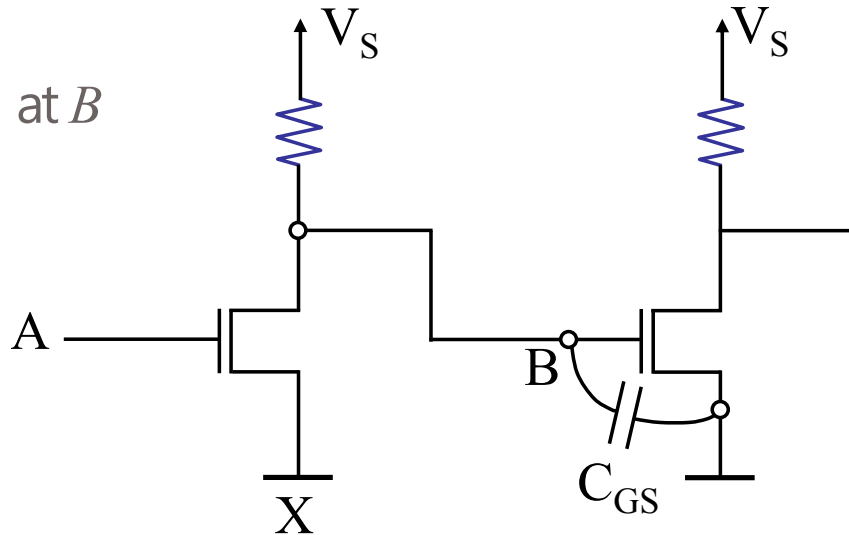


1  $\rightarrow$  0 at A

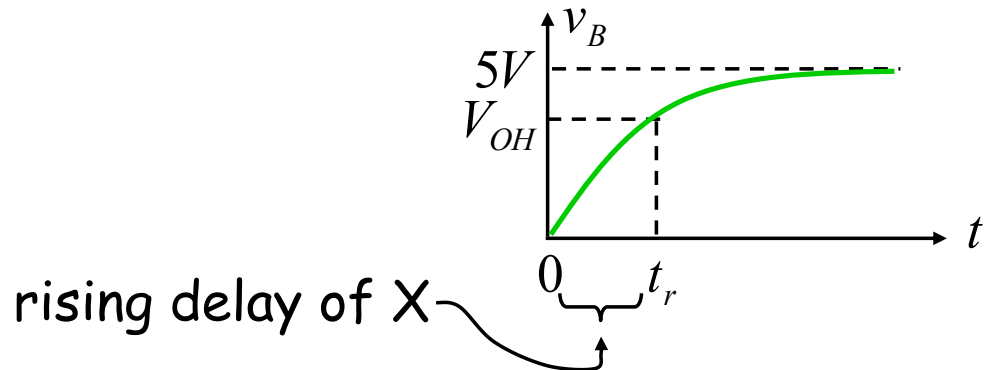

rising delay of X

## Equivalent circuit for 0 → 1 at B

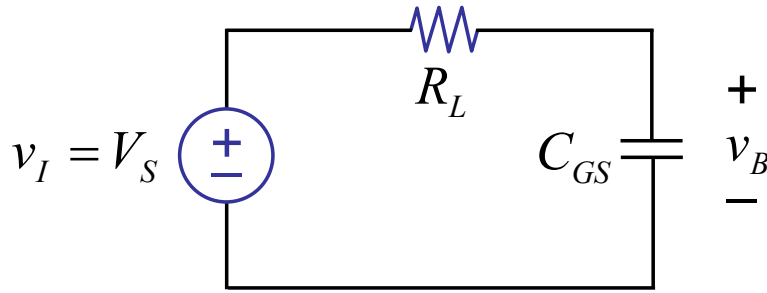

$$v_I = V_S \quad \text{for } t \geq 0$$
$$v_B(0) = 0$$

$$v_B = V_S + (0 - V_S) e^{\frac{-t}{R_L C_{GS}}}$$

Now, we need to find  $t$  for which  $v_B = V_{OH}$ .

$$v_{OH} = V_S - V_S e^{\frac{-t}{R_L C_{GS}}}$$


Find  $t_r$  :

$$V_S e^{\frac{-t_r}{R_L C_{GS}}} = V_S - V_{OH}$$


$$t_r = -R_L C_{GS} \ln \frac{V_S - V_{OH}}{V_S}$$

## Falling Delay
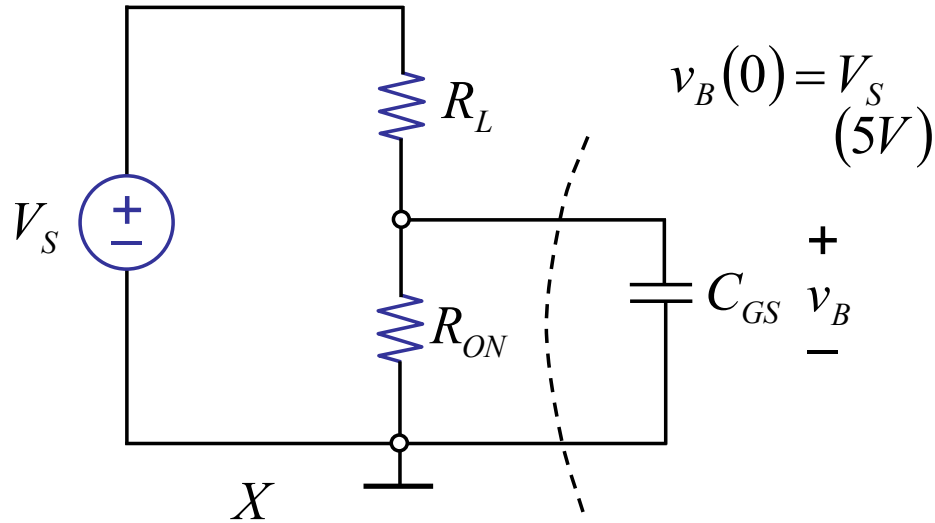
### Equivalent circuit for $1 \rightarrow 0$ at B



Thévenin replacement ...

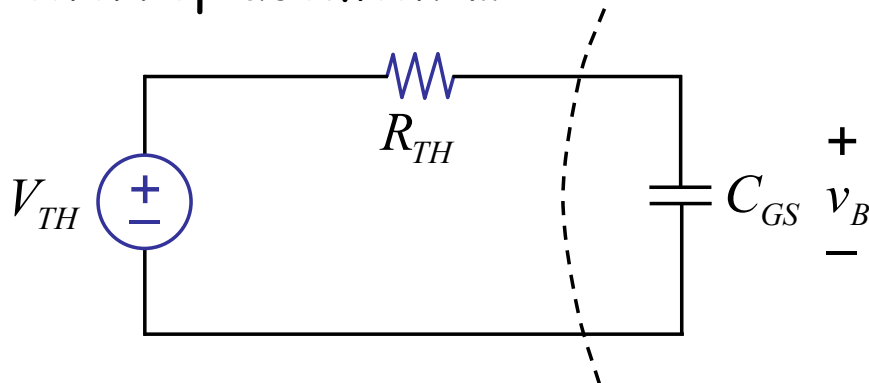





## Falling Delay

$$v_B = V_{TH} + (V_S - V_{TH}) e^{\frac{-t}{R_{TH}C_{GS}}}$$

Falling decay  $t_f$  is the  $t$  for which  $v_B$  falls to  $V_{OL}$

$$V_{OL} = V_{TH} + (V_S - V_{TH}) e^{\frac{-t_f}{R_{TH}C_{GS}}}$$

or

$$t_f = -R_{TH}C_{GS} \ln \frac{V_{OL} - V_{TH}}{V_S - V_{TH}}$$

