






Electrical and Electronics Circuits (4190.206A 002)

- Lecturer: Taehyun Kim (taehyun@snu.ac.kr, 301-407)
- Class hour: Mon. and Wed. 2:00~3:15pm / 301-203
- Reservation for make-up class hour
 - 9/30 (Mon) 7pm-8:15pm
- There will be a class on 10/9 (Wed) Hangul Day, but the class attendance won't be checked, and video recording of the class will become available at ETL.
- Office hour: Mon. 7:00~8:00pm, Wed. 3:30~4:30pm / 301-407 (Please check my schedule before you come to my office)
- TA: Chaewon Kim (kcwchae@gmail.com , 301-416)
- Textbook : "Foundations of Analog and Digital Electronic Circuits"
- Course homepage: ETL
- Grades: 3 exams 30, 30, 30% homework + attendance: 10% (If you cannot attend the class for official reason, please let me or TA know in advance.)
- Self-attendance check



Review

- Associated variable convention
 - Define current to flow in at the device terminal assigned to be positive voltage
 - Never forget to define the polarity of the voltage and the direction of current at the beginning of the circuit analysis.
- I-V characteristics
 - Resistor & diode
 - Voltage source & current source
 - Open and short circuit
- Circuit analysis method
 - Kirchhoff's voltage law (KVL): $\sum_{loop} v_j = 0$ around each loop
 - Kirchhoff's current law (KCL): $\sum_{node} i_j = 0$ at each node

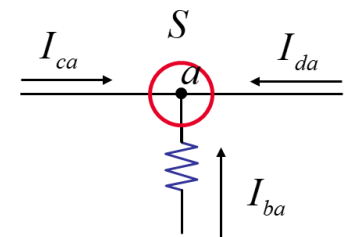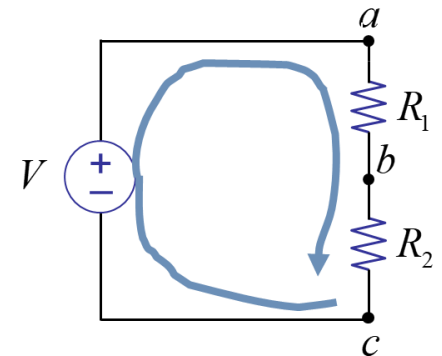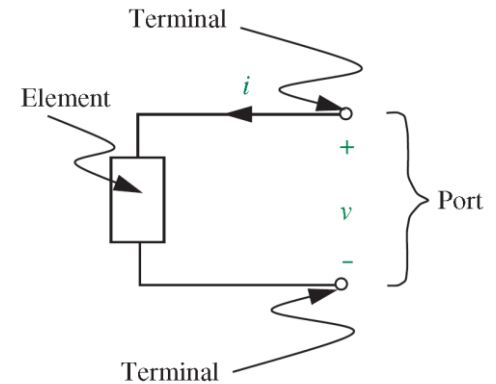




Chap. 2 Resistive Networks

Chap. 3 Network Theorems



- Kirchhoff's Current Law (KCL)
 - Kirchhoff's Voltage Law (KVL)
 - Circuit analysis methods
 - Basic KVL, KCL method (2.3)
 - Node analysis method (3.2 ~ 3.3)
 - Element combination method (2.4)
 - Superposition method (3.5)
 - Thevenin Method (3.6)
 - Norton Method (3.6)
 - 2.6 Dependent Sources and the Control Concept will be discussed later with amplifier
- 



Circuit Analysis Method 1: Basic KVL, KCL method


- Goal: Find all element V 's and I 's
 1. Write element $I - V$ relationships from lumped circuit abstraction
 2. Write KVL for all loops
 3. Write KCL for all nodes
 4. Solve the set of linear equations





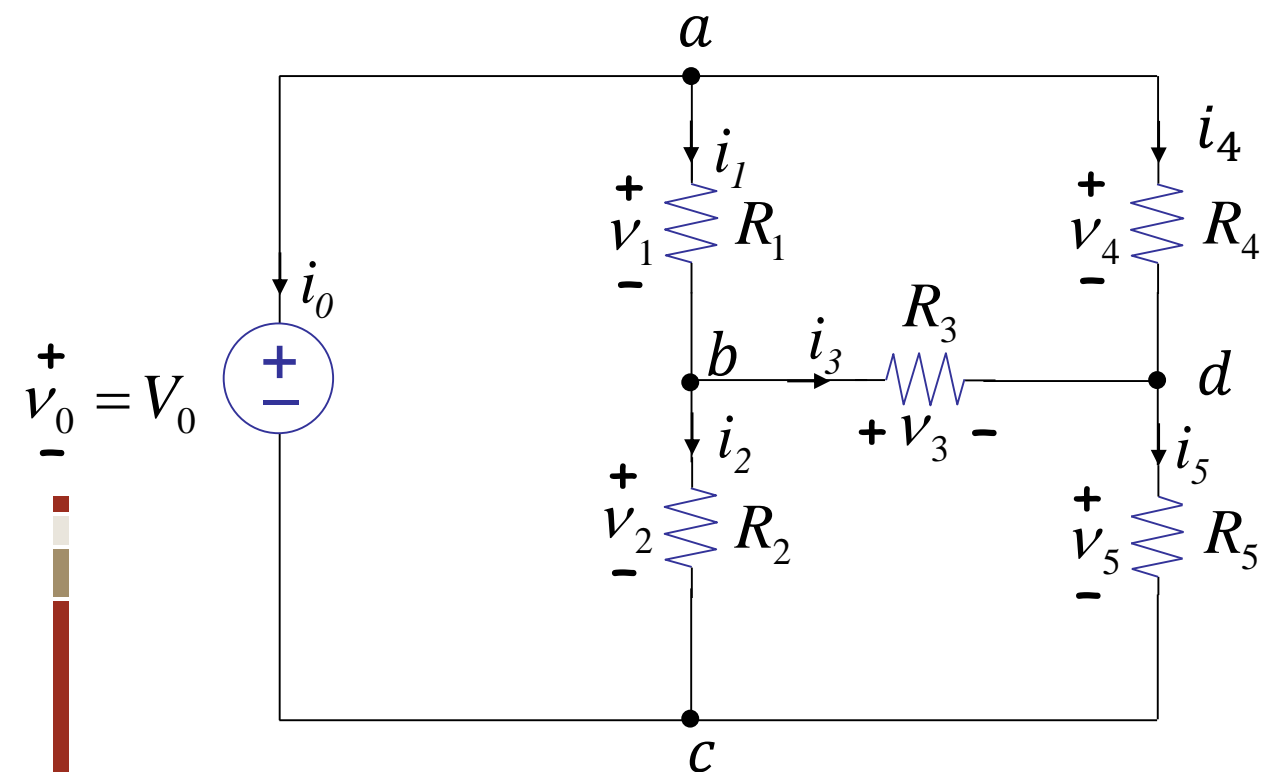Example


- $v_0 \cdots v_5, i_0 \cdots i_5 \Rightarrow 12$ unknowns



Example

$$\begin{aligned} v_0 &= V_0 \leftarrow \text{given} & v_3 &= i_3 R_3 \\ v_1 &= i_1 R_1 & v_4 &= i_4 R_4 \\ v_2 &= i_2 R_2 & v_5 &= i_5 R_5 \end{aligned}$$

- Element relations (v , i)

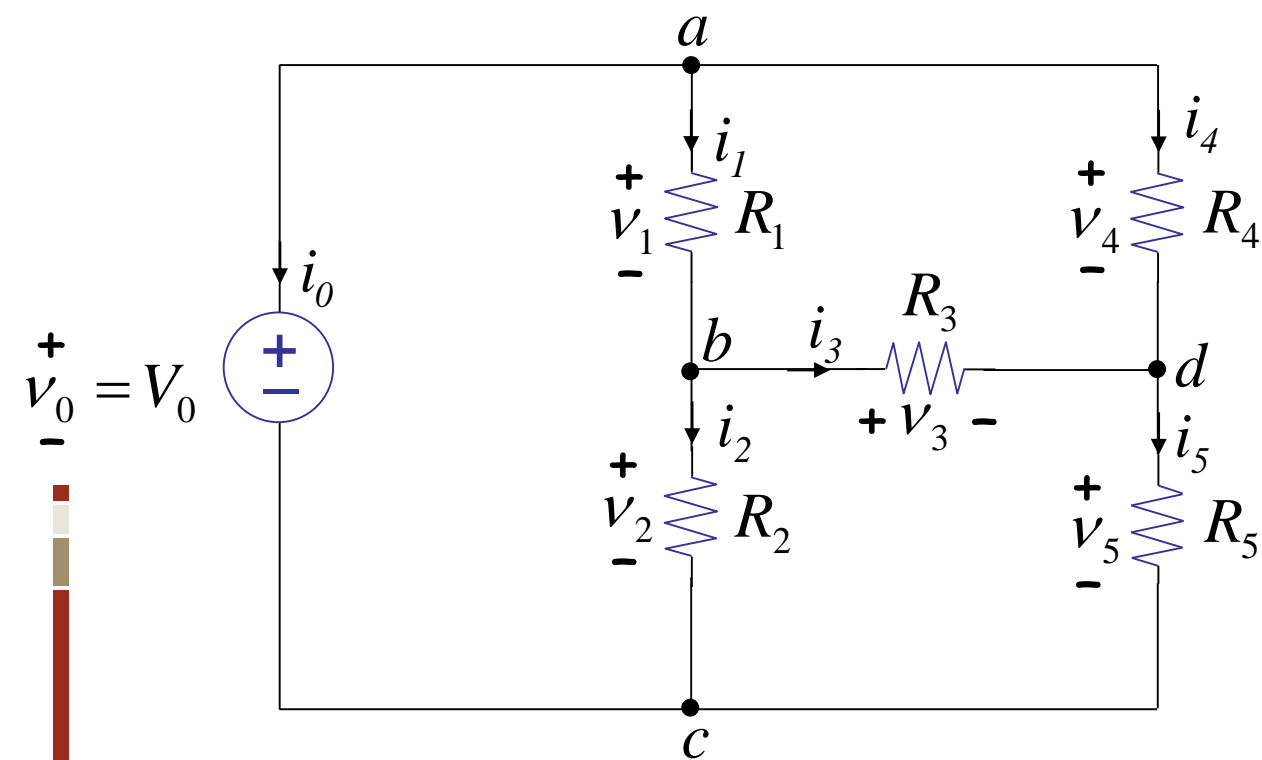

Example

- KVL: as we traverse the loop, if we meet minus terminal, then subtract the voltage, and if we meet plus terminal, add the voltage.

$$- L1: -v_0 + v_1 + v_2 = 0$$

$$- L2: -v_1 + v_4 - v_3 = 0$$

$$- L3: -v_2 + v_3 + v_5 = 0$$


$$- L4: -v_0 + v_4 + v_5 = 0$$

➔ redundant

$$L1 + L2 + L3 \Rightarrow L4$$

If we draw all the loops in clockwise direction, each internal element such as R_1 , R_2 , R_3 appears twice with opposite sign in two elementary loop calculations. Therefore, if we add all the small loops, all the internal elements will cancel out, and the calculation for the outer loop will be obtained.

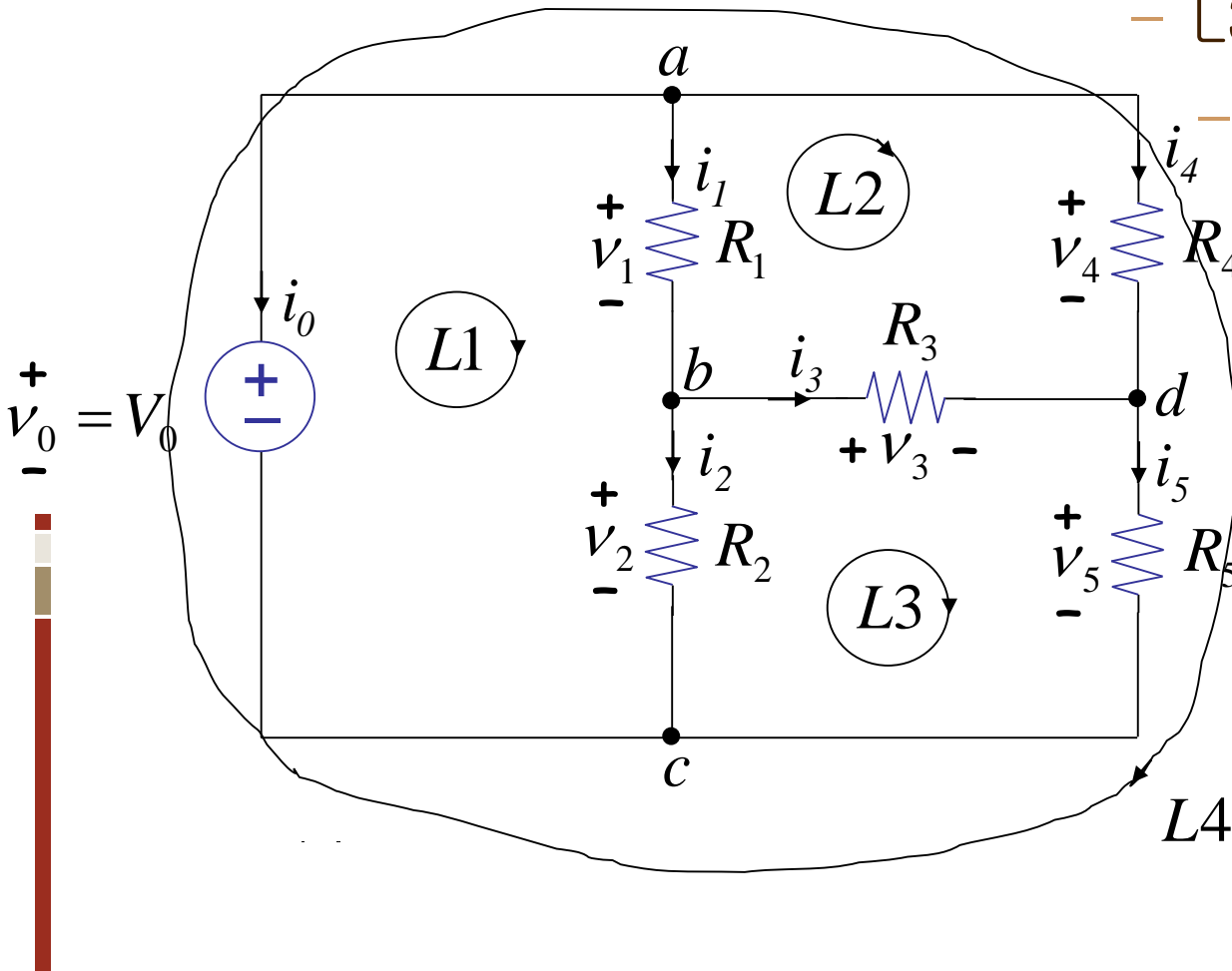Also, the calculation for any other shape of loops can be also obtained by combining several elementary loops.



Example

- KCL

a: $i_0 + i_1 + i_4 = 0$


b: $i_2 + i_3 - i_1 = 0$

d: $i_5 - i_3 - i_4 = 0$

c: $-i_0 - i_2 - i_5 = 0$ redundant

If we add all the outgoing currents at each node except one specific node (e.g. node c), then the same current will appear in two summations with opposite signs except those currents exiting the specific node. Therefore, the summation of all the equations will cancel out all other currents except those currents flowing into the specific node.

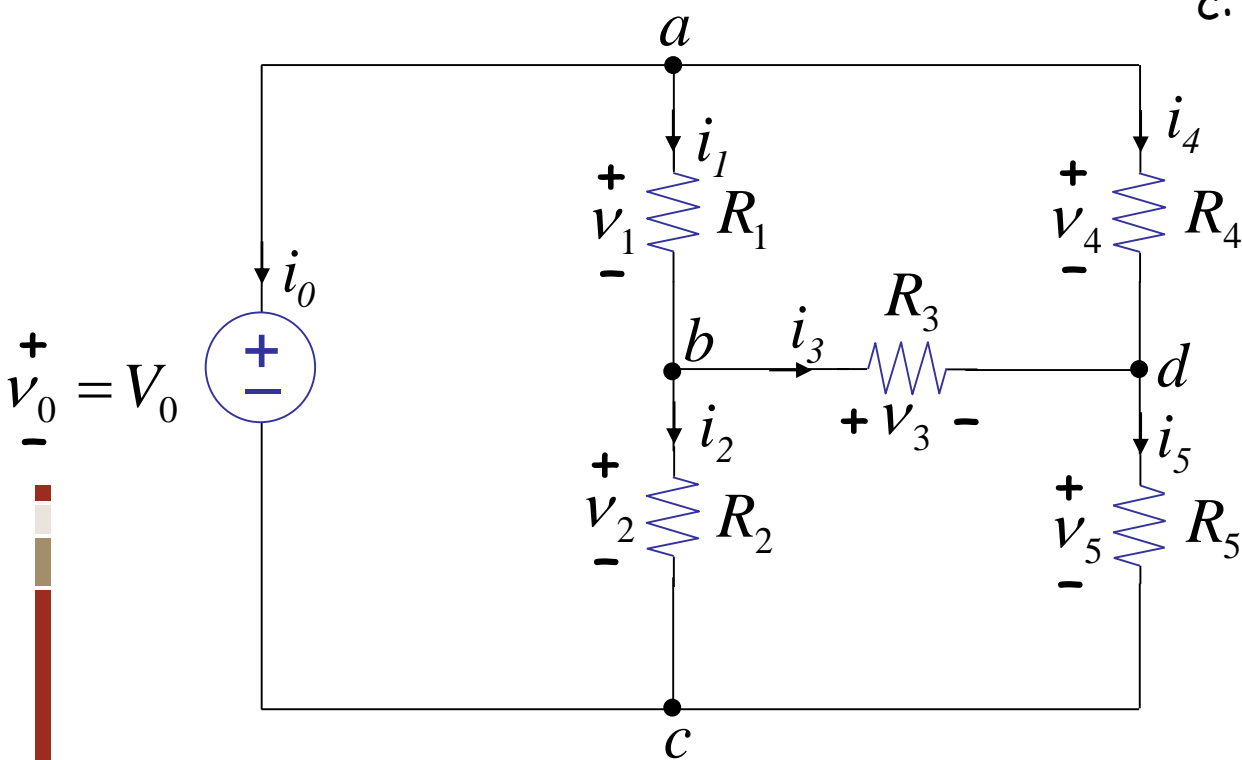In general, there will be always a single node whose KCL equation is redundant.



Example

$v_0, v_1, \dots, v_5, i_0, i_1, \dots, i_5$

12 unknowns

1. Element relations (v, i)

$$v_0 = V_0 \leftarrow \text{given} \quad v_3 = i_3 R_3$$

$$v_1 = i_1 R_1 \quad v_4 = i_4 R_4$$

$$v_2 = i_2 R_2 \quad v_5 = i_5 R_5$$

6 equations

12 equations

2. KVL for loops

$$\text{L1: } -v_0 + v_1 + v_2 = 0$$

$$\text{L2: } -v_1 + v_4 - v_3 = 0$$

$$\text{L3: } -v_2 + v_3 + v_5 = 0$$

$$\text{L4: } -v_0 + v_4 + v_5 = 0 \leftarrow \text{redundant}$$

3 independent equations

3. KCL at nodes

$$\text{a: } i_0 + i_1 + i_4 = 0$$

$$\text{b: } -i_1 + i_2 + i_3 = 0$$

$$\text{d: } -i_3 - i_4 + i_5 = 0$$

$$\text{c: } -i_0 - i_2 - i_5 = 0 \leftarrow \text{redundant}$$

3 independent equations

Derivation of node analysis method

- How to solve 12 equations?
 - Unknowns: $v_0, v_1, \dots, v_5, i_0, i_1, \dots, i_5$
 - Remove all currents with elements relations

1. Element relations (v, i)

$$v_0 = V_0 \quad v_3 = i_3 R_3$$

$$v_1 = i_1 R_1 \quad v_4 = i_4 R_4$$

$$v_2 = i_2 R_2 \quad v_5 = i_5 R_5$$

2. KCL at nodes

a: $i_0 + i_1 + i_4 = 0$

b: $-i_1 + i_2 + i_3 = 0$

d: $-i_3 - i_4 + i_5 = 0$

c: $-i_0 - i_2 - i_5 = 0$ ← redundant


3. KVL for loops

L1: $-v_0 + v_1 + v_2 = 0$

L2: $-v_1 + v_4 - v_3 = 0$


L3: $-v_2 + v_3 + v_5 = 0$

L4: $-v_0 + v_4 + v_5 = 0$ ← redundant

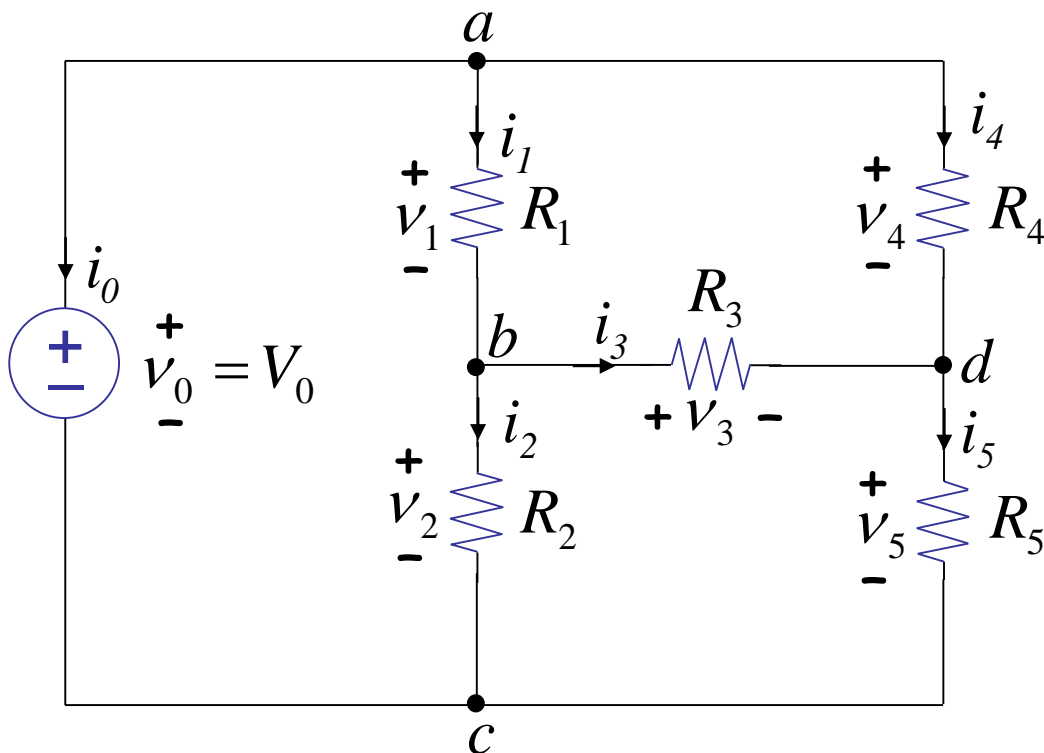

Derivation of node analysis method

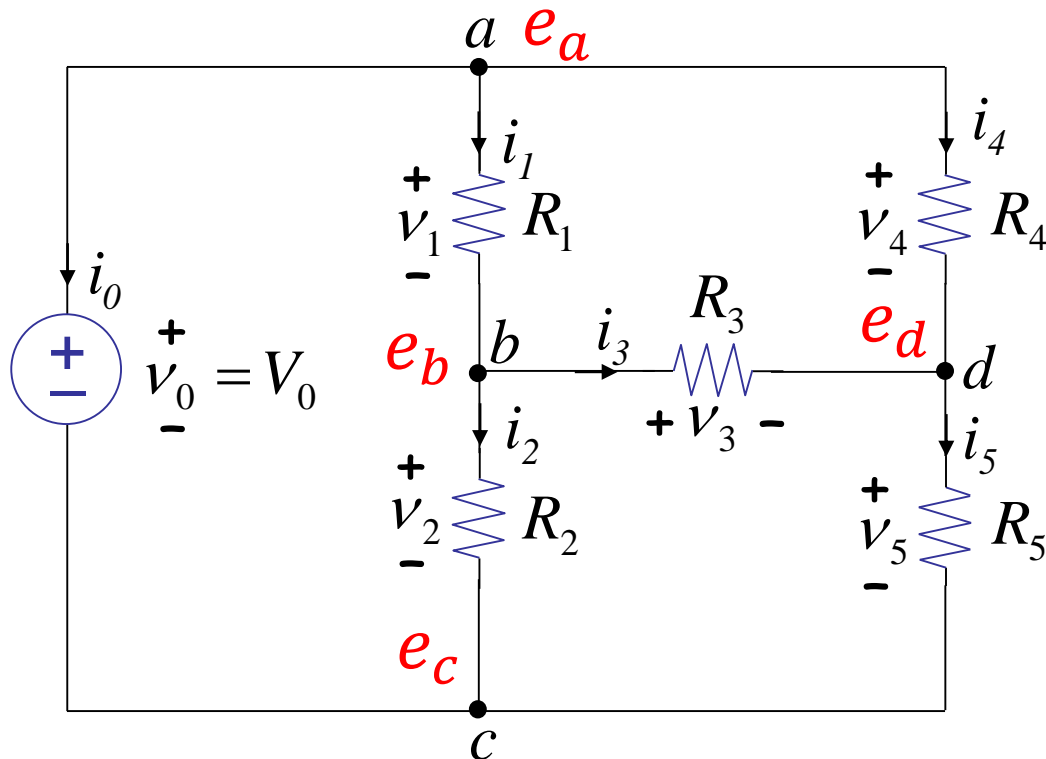- How to solve 12 equations?
 - Unknowns: $v_0, v_1, \dots, v_5, i_0, i_1, \dots, i_5$
 - Remove all currents with elements relations \rightarrow 5 voltages + 1 current
 - Define node voltage rather than voltage across each element. \rightarrow Automatically satisfy the KVL eqs.



1. Element relations (v, i)

~~$$\begin{aligned}
 v_0 &= V_0 & v_3 &= i_3 R_3 \\
 v_1 &= i_1 R_1 & v_4 &= i_4 R_4 \\
 v_2 &= i_2 R_2 & v_5 &= i_5 R_5
 \end{aligned}$$~~

2. KCL at nodes

$$\begin{aligned}
 \text{a: } i_0 + v_1/R_1 + v_4/R_4 &= 0 \\
 \text{b: } -v_1/R_1 + v_2/R_2 + v_3/R_3 &= 0 \\
 \text{d: } -v_3/R_3 - v_4/R_4 + v_5/R_5 &= 0 \\
 \text{c: } -i_0 - i_2 - i_5 &= 0 \leftarrow \text{redundant}
 \end{aligned}$$


3. KVL for loops

~~$$\begin{aligned}
 \text{L1: } -v_0 + v_1 + v_2 &= 0 \\
 \text{L2: } -v_1 + v_3 + v_4 &= 0 \\
 \text{L3: } -v_2 + v_3 + v_5 &= 0 \\
 \text{L4: } -v_0 + v_4 + v_5 &= 0 \leftarrow \text{redundant}
 \end{aligned}$$~~

$$\begin{aligned}
 \text{E.g. L1 loop: } & -v_0 + v_1 + v_2 \\
 &= -(e_a - e_c) + (e_a - e_b) + (e_b - e_c) \\
 &= 0
 \end{aligned}$$

Derivation of node analysis method

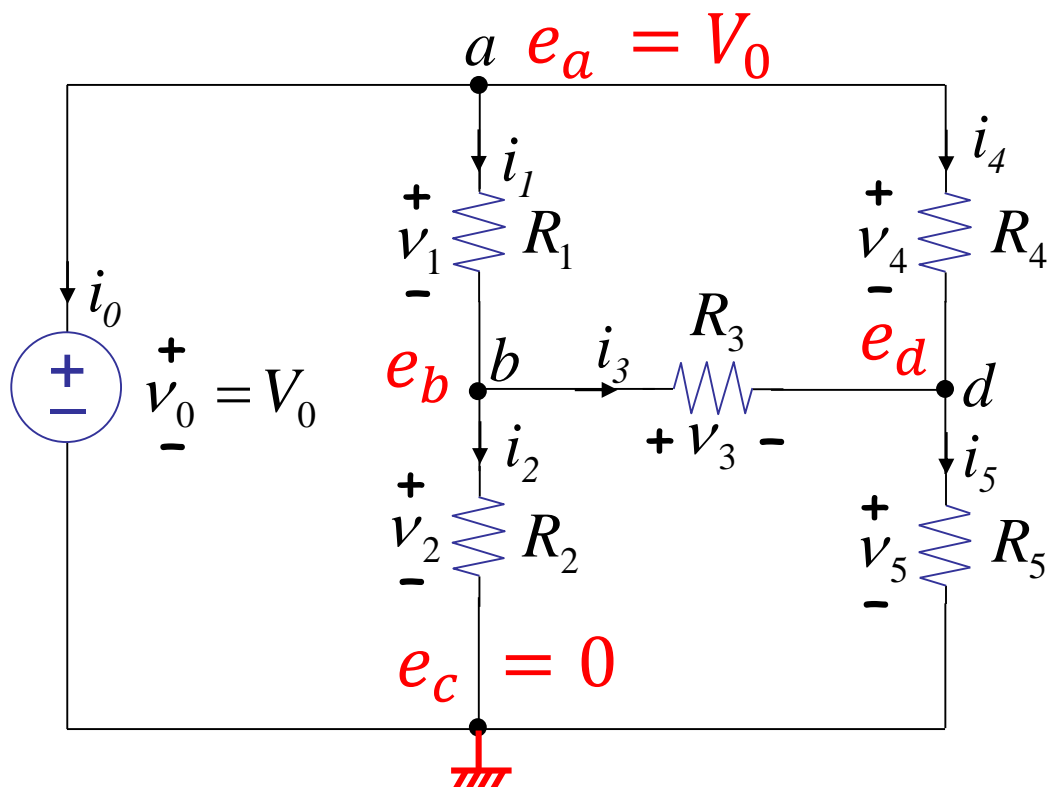- Unknown 4 voltages and one current
- We have a freedom to choose one of the voltages as ground. E.g. $v_c = 0$.
- When a node is connected to the ground through a voltage source, voltage of that node will be fixed, e.g. $v_a = V_0$ and we don't need to solve the KCL at that node.
- Problem is reduced to find two unknown voltages e_b and e_d .



2. KCL at nodes

a: ~~$i_0 + v_1/R_1 + v_4/R_4 = 0$~~

b: $-v_1/R_1 + v_2/R_2 + v_3/R_3 = 0$

d: $-v_3/R_3 - v_4/R_4 + v_5/R_5 = 0$

By using

□ $v_1 = e_a - e_b = V_0 - e_b$

□ $v_2 = e_b - e_c = e_b$

□ $v_3 = e_b - e_d$

□ $v_4 = e_a - e_d = V_0 - e_d$

□ $v_5 = e_d - e_c = e_d$


KCL at nodes turns into

b: $-\frac{(V_0 - e_b)}{R_1} + \frac{e_b}{R_2} + \frac{(e_b - e_d)}{R_3} = 0$


d: $-\frac{(e_b - e_d)}{R_3} - \frac{(V_0 - e_d)}{R_4} + \frac{e_d}{R_5} = 0$




Circuit Analysis Method 3: Node analysis

- KCL at nodes using V's referenced w.r.t. ground
 1. Select reference node ( ground) from which voltages are measured.
 2. Label voltages of remaining nodes with respect to ground. These are the primary unknowns.
 3. Write KCL for all but the ground node, substituting device laws.
 4. For nodes directly connected to terminals of voltage sources, write down the voltage drop relation (KVL).
 5. Solve for node voltages.
 6. Back solve for branch voltages and currents (i.e., the secondary unknowns)
- Exceptional case happens with a floating independent voltage source at step 3. Check section 3.3.2 of the text for the solution.

Circuit Analysis Method 3: Node analysis

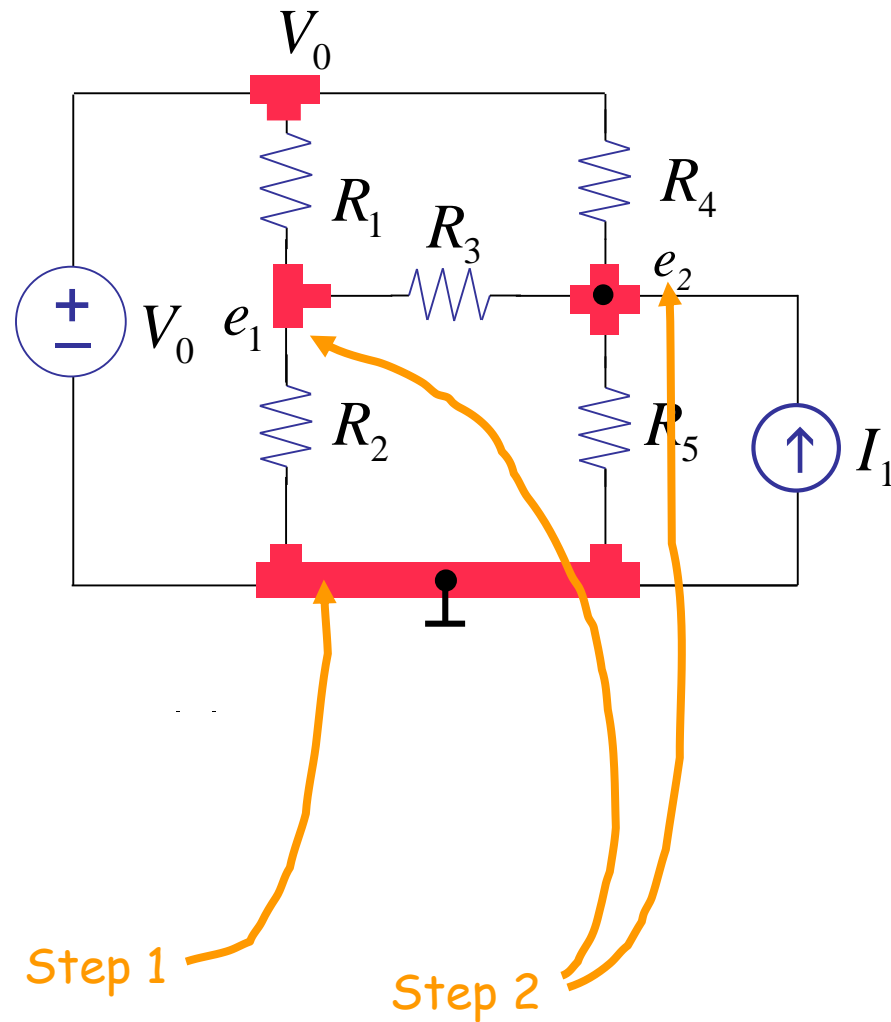

Circuit Analysis Method 3: Node analysis

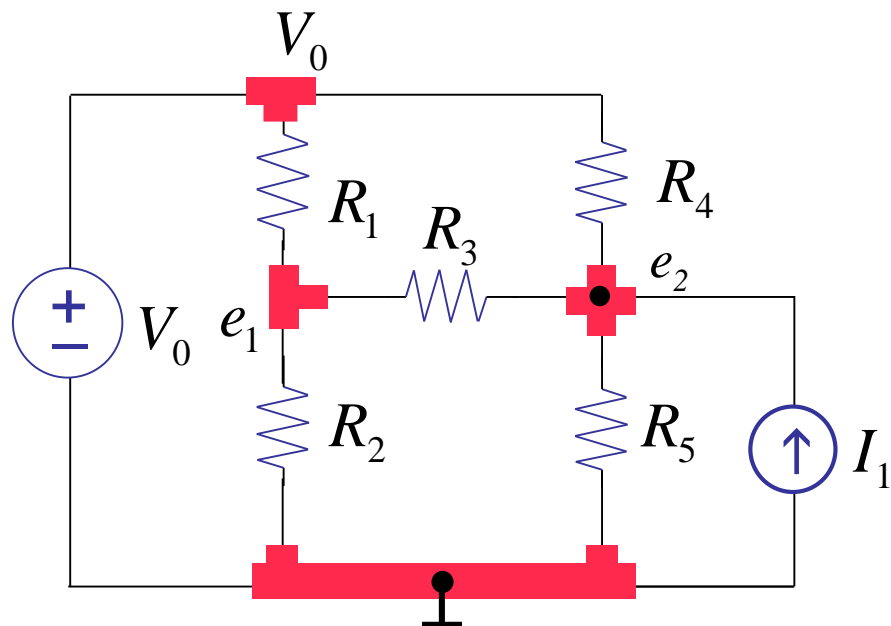

for
convenience,
write

$$G_i = \frac{1}{R_i}$$

Step 3


KCL at e_1

$$(e_1 - V_0)G_1 + (e_1 - e_2)G_3 + (e_1)G_2 = 0$$

KCL at e_2

$$(e_2 - e_1)G_3 + (e_2 - V_0)G_4 + (e_2)G_5 - I_1 = 0$$

Circuit Analysis Method 3: Node analysis

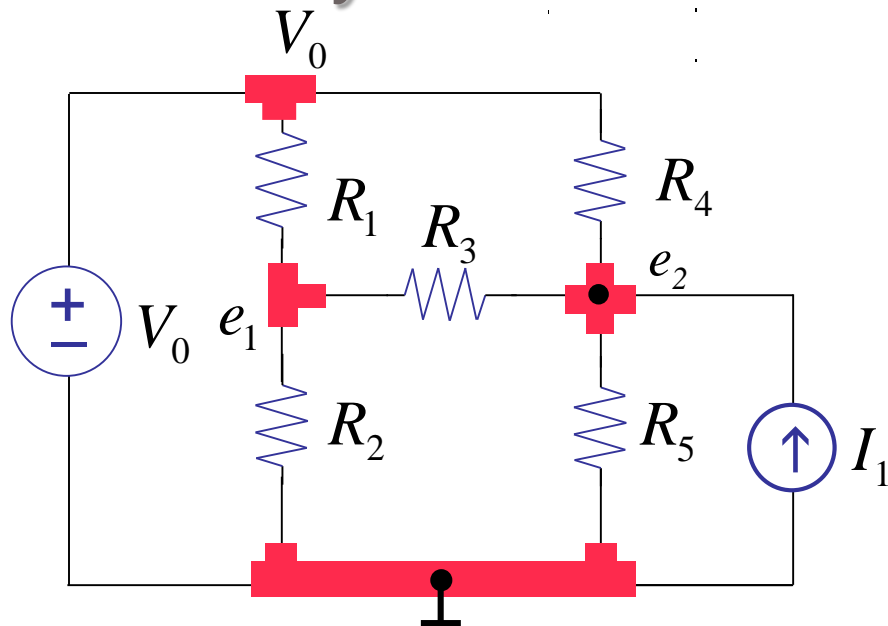

$$G_i = \frac{1}{R_i}$$

KCL at e_1 $(e_1 - V_0)G_1 + (e_1 - e_2)G_3 + (e_1)G_2 = 0$

KCL at e_2 $(e_2 - e_1)G_3 + (e_2 - V_0)G_4 + (e_2)G_5 - I_1 = 0$

move constant terms to RHS & collect unknowns

$$e_1(G_1 + G_2 + G_3) + e_2(-G_3) = V_0(G_1)$$

$$e_1(-G_3) + e_2(G_3 + G_4 + G_5) = V_0(G_4) + I_1$$

2 equations, 2 unknowns \longrightarrow Solve for e 's

Step 4

Circuit Analysis Method 3: Node analysis

In matrix form:

$$\left[\begin{array}{c|c} G_1 + G_2 + G_3 & -G_3 \\ \hline -G_3 & G_3 + G_4 + G_5 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1 V_0 \\ G_4 V_0 + I_1 \end{bmatrix}$$

conductance matrix
unknown node voltages
sources

Solve



$$\begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \frac{\left[\begin{array}{c|c} G_3 + G_4 + G_5 & G_3 \\ \hline G_3 & G_1 + G_2 + G_3 \end{array} \right] \begin{bmatrix} G_1 V_0 \\ G_4 V_0 + I_1 \end{bmatrix}}{(G_1 + G_2 + G_3)(G_3 + G_4 + G_5) - G_3^2}$$

$$e_1 = \frac{(G_3 + G_4 + G_5)(G_1 V_0) + (G_3)(G_4 V_0 + I_1)}{G_1 G_3 + G_1 G_4 + G_1 G_5 + G_2 G_3 + G_2 G_4 + G_2 G_5 + G_3^2 + G_3 G_4 + G_3 G_5}$$



$$e_2 = \frac{(G_3)(G_1 V_0) + (G_1 + G_2 + G_3)(G_4 V_0 + I_1)}{G_1 G_3 + G_1 G_4 + G_1 G_5 + G_2 G_3 + G_2 G_4 + G_2 G_5 + G_3^2 + G_3 G_4 + G_3 G_5}$$

(same denominator)

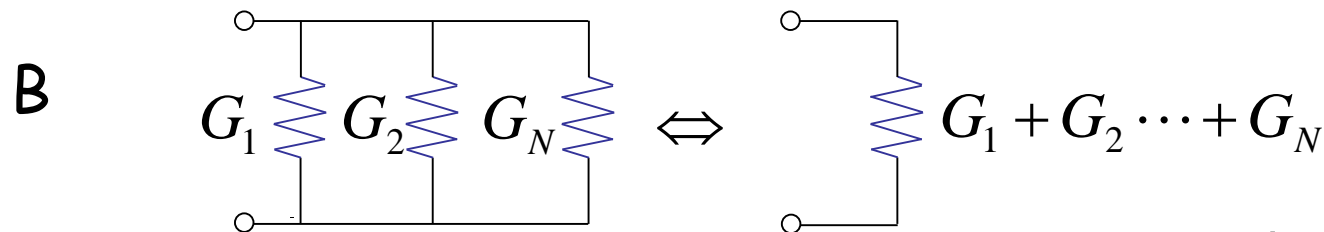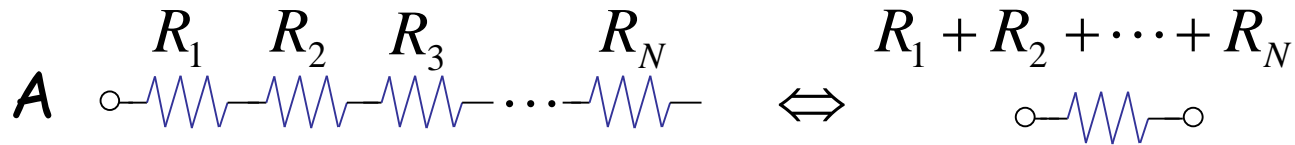Circuit Analysis Method 2: Apply element combination rules




Conductance $G_i \equiv \frac{1}{R_i}$

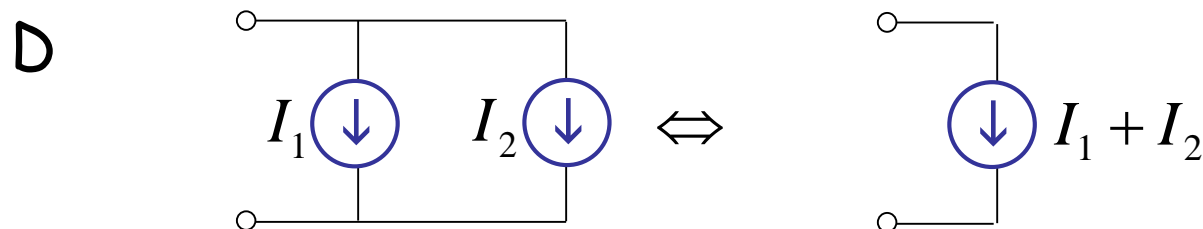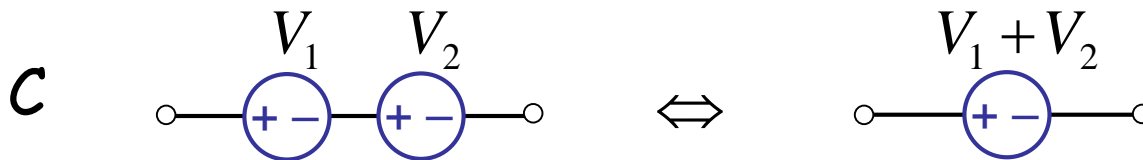

Voltage divider

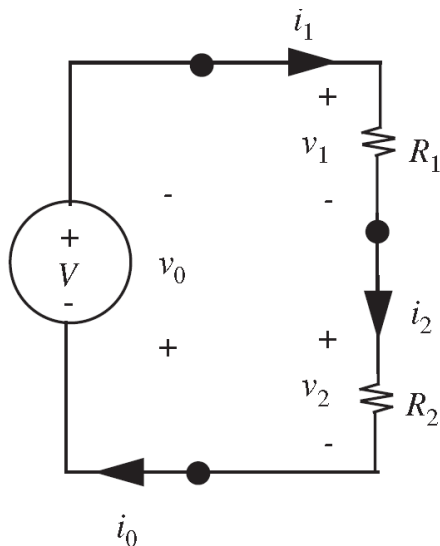- The only constraint: current should be the same



1. Element laws

$$v_0 = -V$$

$$v_1 = R_1 i_1$$

$$v_2 = R_2 i_2$$

3. KVL

$$v_0 + v_1 + v_2 = 0$$

2. KCL

$$-i_0 + i_1 = 0$$

$$-i_1 + i_2 = 0$$

4. Solve the equations


$$i_0 = i_1 = i_2 = \frac{V}{R_1 + R_2}$$

From the relation between the voltage V and current i_0 from the voltage source, we can conclude that the equivalent resistance R_{total} of two resistors connected in series is $R_1 + R_2$.

What is the voltage v_2 across R_2 ?


$$v_2 = i_2 R_2 = \frac{V}{R_1 + R_2} R_2 = \frac{R_2}{R_1 + R_2} V$$

➔ Voltage divider

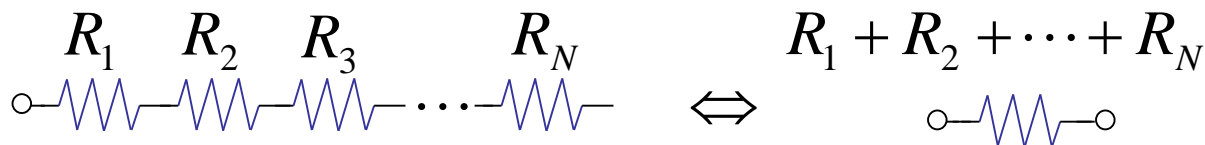


Voltage drop

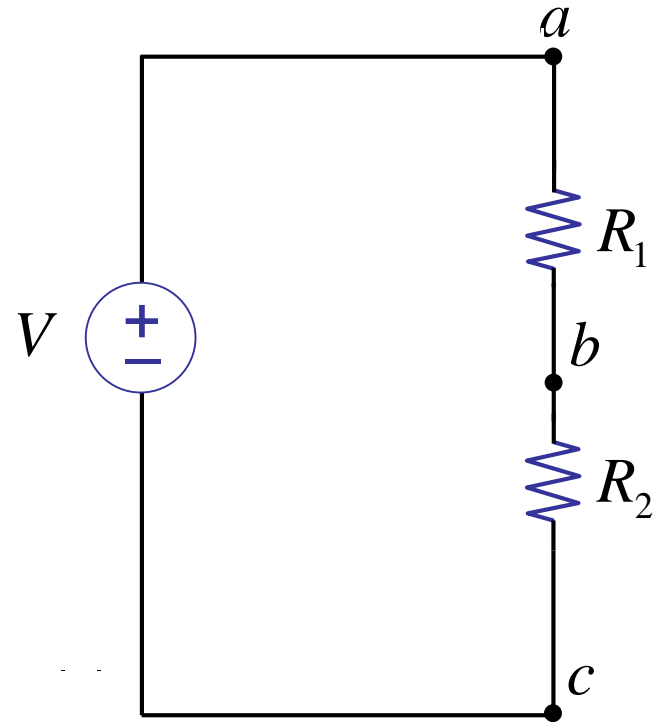- “Voltage drop” is one of the most frequently used terminologies in the class, so get used to it.
- “Voltage drop” across R_1
- “Voltage drop” across R_2
- “Voltage drop” across voltage source



Current divider

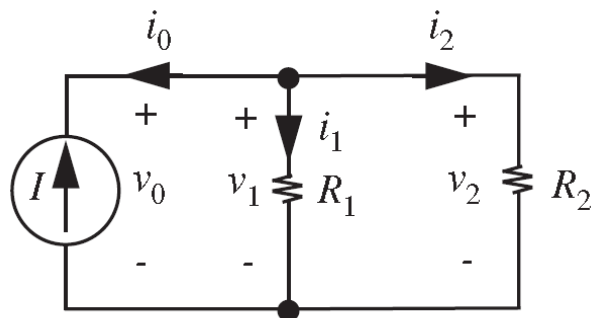

1. Element laws

$$\begin{aligned} i_0 &= -I \\ v_1 &= R_1 i_1 \\ v_2 &= R_2 i_2 \end{aligned}$$

2. KVL

$$\begin{aligned} -v_0 + v_1 &= 0 \\ -v_1 + v_2 &= 0 \end{aligned}$$

3. KCL

$$i_0 + i_1 + i_2 = 0$$

4. Solve the equations

$$v_0 = v_1 = v_2 = \frac{I}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{I}{G_1 + G_2}$$


Conductance
 $G_i \equiv 1/R_i$

From the relation between the voltage v_0 and current i_0 from the current source, we can conclude that the equivalent resistance R_{total} of two resistors connected in parallel is $\left(\frac{1}{R_1} + \frac{1}{R_2}\right)^{-1}$. Or equivalently, $G_{total} = G_1 + G_2$.

What is the current i_2 across R_2 ?


$$i_2 = \frac{v_2}{R_2} = \frac{I}{R_2 \left(\frac{1}{R_1} + \frac{1}{R_2}\right)} = \frac{R_1}{R_2 + R_1} I$$

➔ Current divider

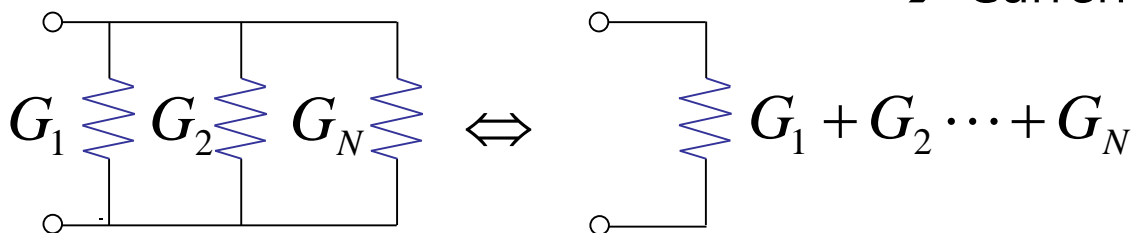

Circuit Analysis Method 2: Apply element combination rules

- Example

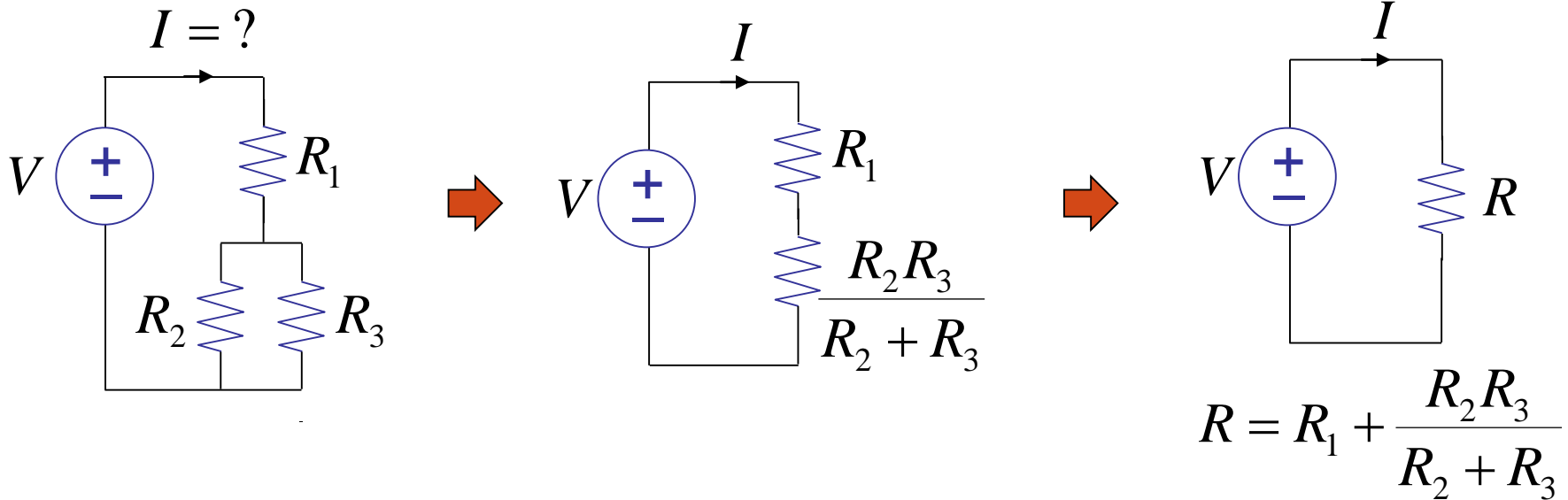

$$I = \frac{V}{R}$$



Summary

- Various circuit analysis methods
 - Method 1: Basic KVL $\sum_{loop} V_i = 0$ and KCL $\sum_{node} I_i = 0$
 - Method 2: Elementary combination method
 - $R_{total} = \sum_{series} R_i$ for series resistors
 - $G_{total} = \sum_{parallel} G_i$ for parallel resistors where $G_i = 1/R_i$
 - Method 3: Node analysis method
 - Define voltage variables e_j at each node j except ground
 - Apply KCL at each node j while using " $(e_j - e_i)/R_{ij}$ " as the current flowing through the branch between node j and node i .
- Forthcoming
 - Superposition method and linearity
 - Thevenin equivalent circuits