



Electrical and Electronics Circuits (4190.206A 002)

- HW Problem 1-6: the resistance values were missing, and now it is updated as 4R, 2R, R. Please check the updated file.
- HW #1 is due on Oct. 7, 2019 3:15pm
- Make-up class
 - 9/30 (Mon) 7pm-8:15pm (the class attendance won't be checked, and video recording of the class will become available at ETL)
 - There will be still a regular class between 2:00pm~3:15pm on 9/30 (Mon)
- 1st mid-term exam: 10/21(Mon) or 10/23(Wed)
- 2nd mid-term exam: 11/13(Wed) or 11/18(Mon)
- Final exam: 12/11 (Wed) 2:00pm~3:15pm
- There will be a class on 10/9 (Wed) Hangul Day, but the class attendance won't be checked, and video recording of the class will become available at ETL.
- Grades: 3 exams 30, 30, 30% homework + attendance: 10% (If you cannot attend the class for official reason, please let me or TA know in advance.)
- Self-attendance check



Review

■ Digital abstraction

- Why go from analog to digital?
- Definition of forbidden region, $V_{OH}, V_{OL}, V_{IH}, V_{IL}$
- Static discipline


■ Binary logic

- Binary number representation
- AND, OR, NOT, NAND, NOR gates
- Desired truth table \rightarrow sum-of-products, then use simplification relations \leftarrow using OR
- Implementation of logic gates using combination of digital switches and voltage drop across resistors \rightarrow NOT, NAND, NOR and many other combinations


■ MOSFET

- Metal-Oxide Semiconductor Field-Effect Transistor
- S model ("Switch" model): V_{GS} vs. V_T

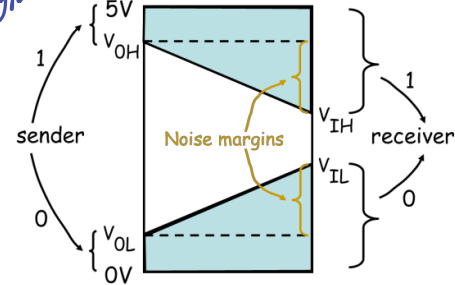even if there exist some noise, the signal will be accepted as 0 or 1.



$$\frac{V_{drop}}{R_L} = 0.$$

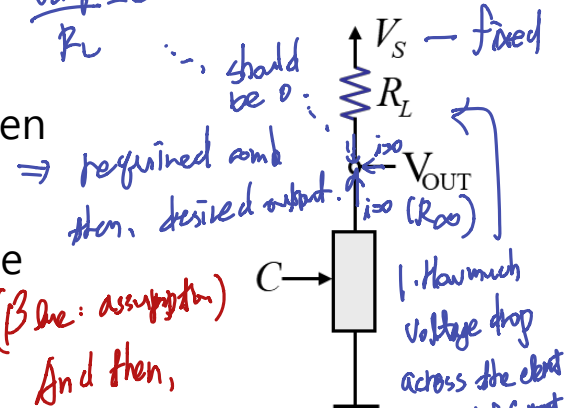

2. ideal assumption, there won't any current across the path $V_{out} \rightarrow$ fixed.

Goal: deliver analog signal to other.

Goal
 - problem: noise.
 - need ways to interface

Analogy → ADC → Computer digital → DAC → Analogy

voltage → discrete → voltage.

0V → 25°C

00010 → 1V 1V → 25°C.

111 → 7V 0.7V

Analog-Digital Conversion

- Motivation for digital abstraction
 - Analog signals are too noisy
 - ➔ Convert the analog signals to digital values and transmit the digital values
 - ➔ Process (or calculate) digital values
 - ➔ Then what? E.g. change of the room temperature, music playing, change of the LED brightness, video playing, self-driving car, communication, printer, ... almost everything connected to the digital device works in the analog world


- Digital device requires a way to interface with the analog world

- Analog-to-digital converter (ADC)
- Digital-to-analog converter (DAC)

- In one of your HW problems, you will see how to implement DAC using a simple resistor network.

- Implementation of ADC

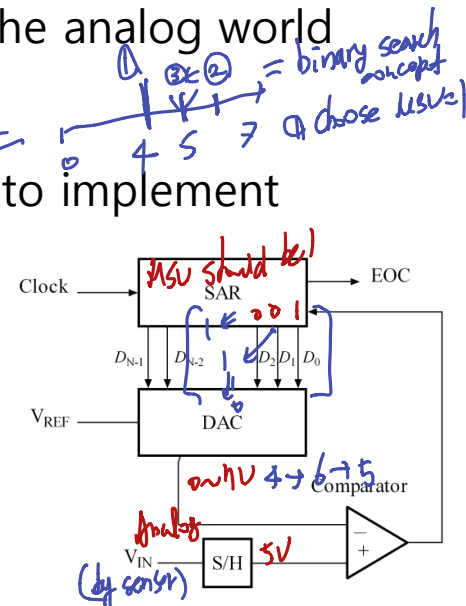- Successive approximation register (SAR) ADC
- Implemented with the help of digital controller



As increasing resolution
 n (lines) ↑ time needed


0.1V
0.1V
0.1V

case ① 0.7V (0.1V)

MOSFET Device Structure

- Metal-Oxide Semiconductor Field-Effect Transistor
- PN junction
- Resistance between S and D:

$$R_{ON} = R_n \frac{L}{W}$$

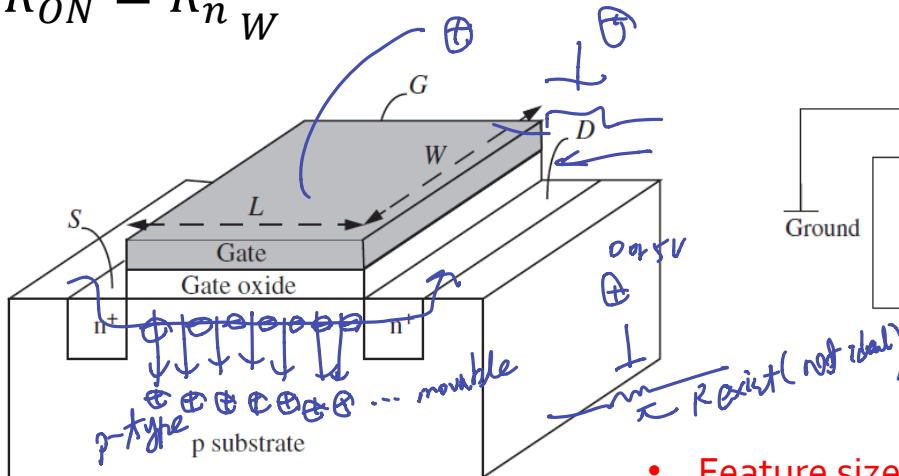

- Feature size
- Moore's law


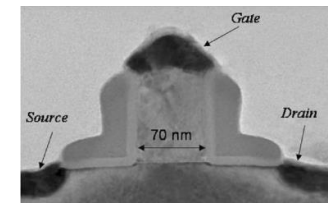
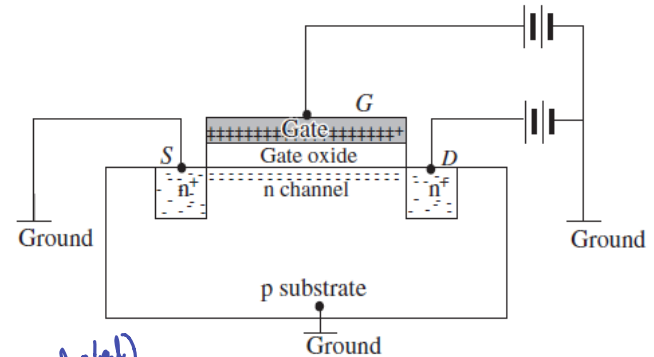
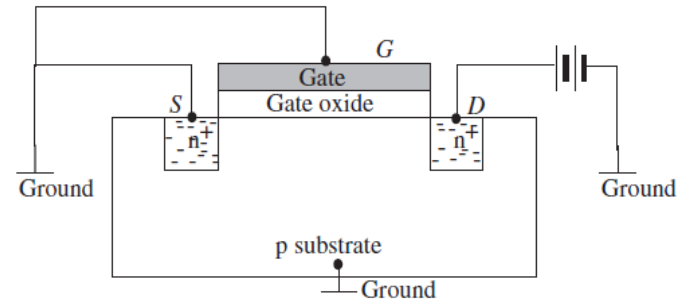



FIGURE 6.38 A cross-sectional picture of Intel's 0.13- μm generation logic transistor.

Switch Resistor (SR) Model of MOSFET

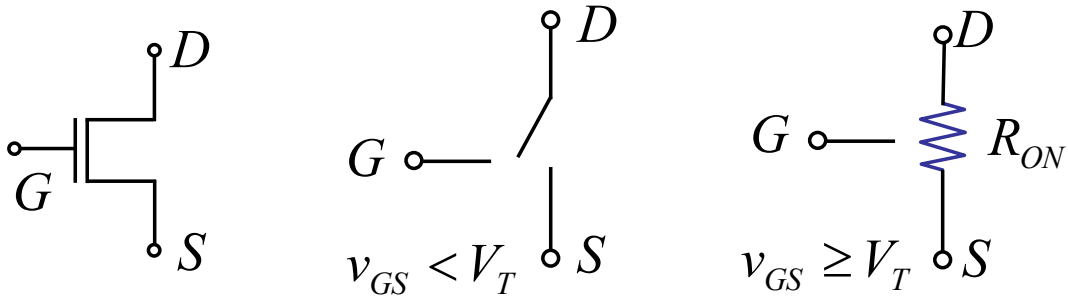
- When MOSFET switch is turned on, there is resistance
- For example, $R_{ON} = 1k\Omega$





MOSFET
S model

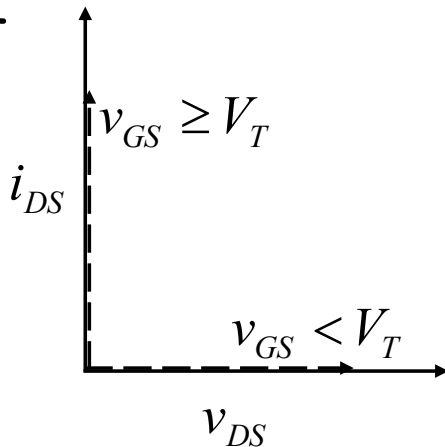

MOSFET
SR model

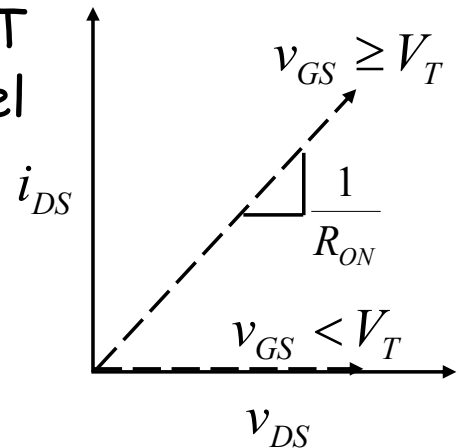

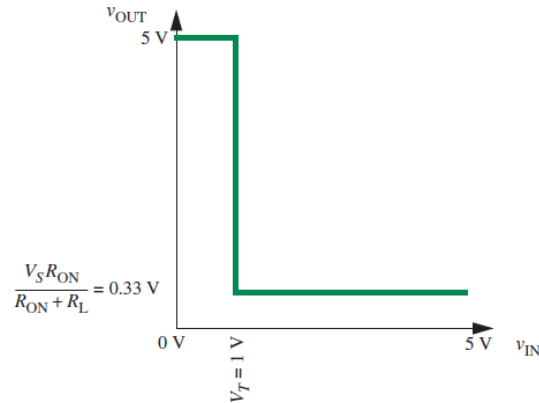
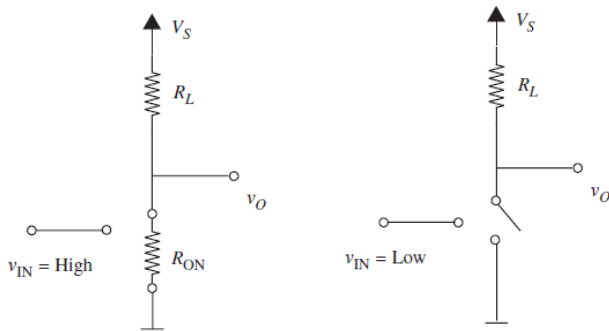
What Determines Resistor Value in Inverter?




- When $v_{IN} = \text{High}$, $v_{OUT} = V_S \frac{R_{ON}}{R_{ON} + R_L}$
- If $V_S = 5\text{V}$, $V_T = 1\text{V}$, $R_{ON} = 1\text{k}\Omega$, $R_L = 14\text{k}\Omega$, $v_{OUT} = 0.33\text{V}$



Pull-up and Pull-down Resistors

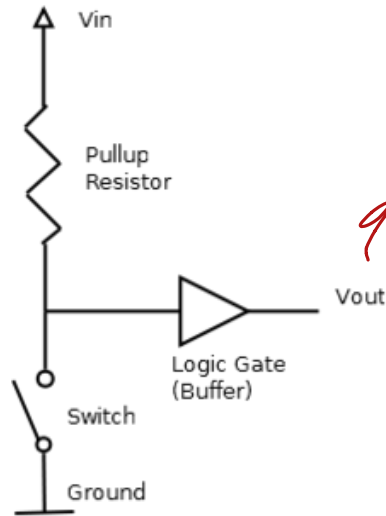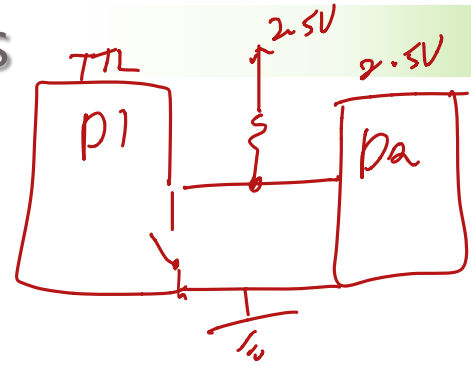


0 or V_{dd}

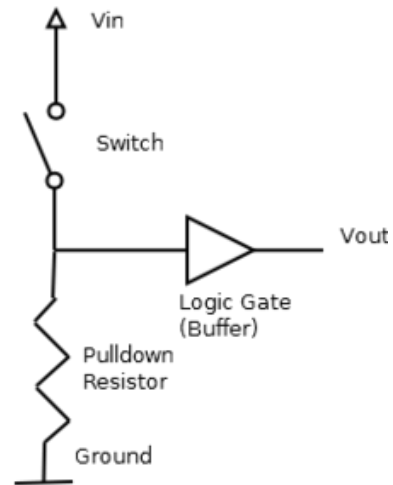

Why Nonlinear Circuits?



■ Diode

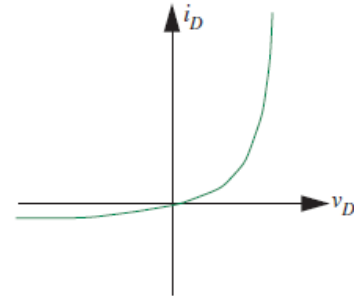- $i_D = I_S(e^{v_D/V_{TH}} - 1)$ where I_S is typically $10^{-12}A$ and V_{TH} is typically $0.025V$



■ MOSFET with gate and drain tied together
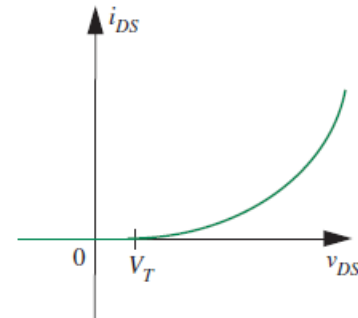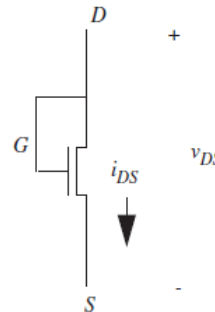
$$i_{DS} = \begin{cases} \frac{K(v_{DS} - V_T)^2}{2} & \text{for } v_{DS} \geq V_T \\ 0 & \text{for } v_{DS} < V_T \end{cases}$$




For the next several lectures...

- Goal: show how to implement amplifier using MOSFET
- Chap. 4 Analysis of Nonlinear Circuits
 - Analytical Solutions (4.2)
 - Graphical Analysis (4.3)
 - Piecewise Linear Analysis (4.4)
 - Incremental Analysis (4.5)
- Chap. 7 The MOSFET Amplifier
 - Large-Signal Analysis of the MOSFET Amplifier (7.6)
 - Operating Point Selection (7.7)
- Chap. 8 The Small-Signal Model



Hypothetical Nonlinear Element

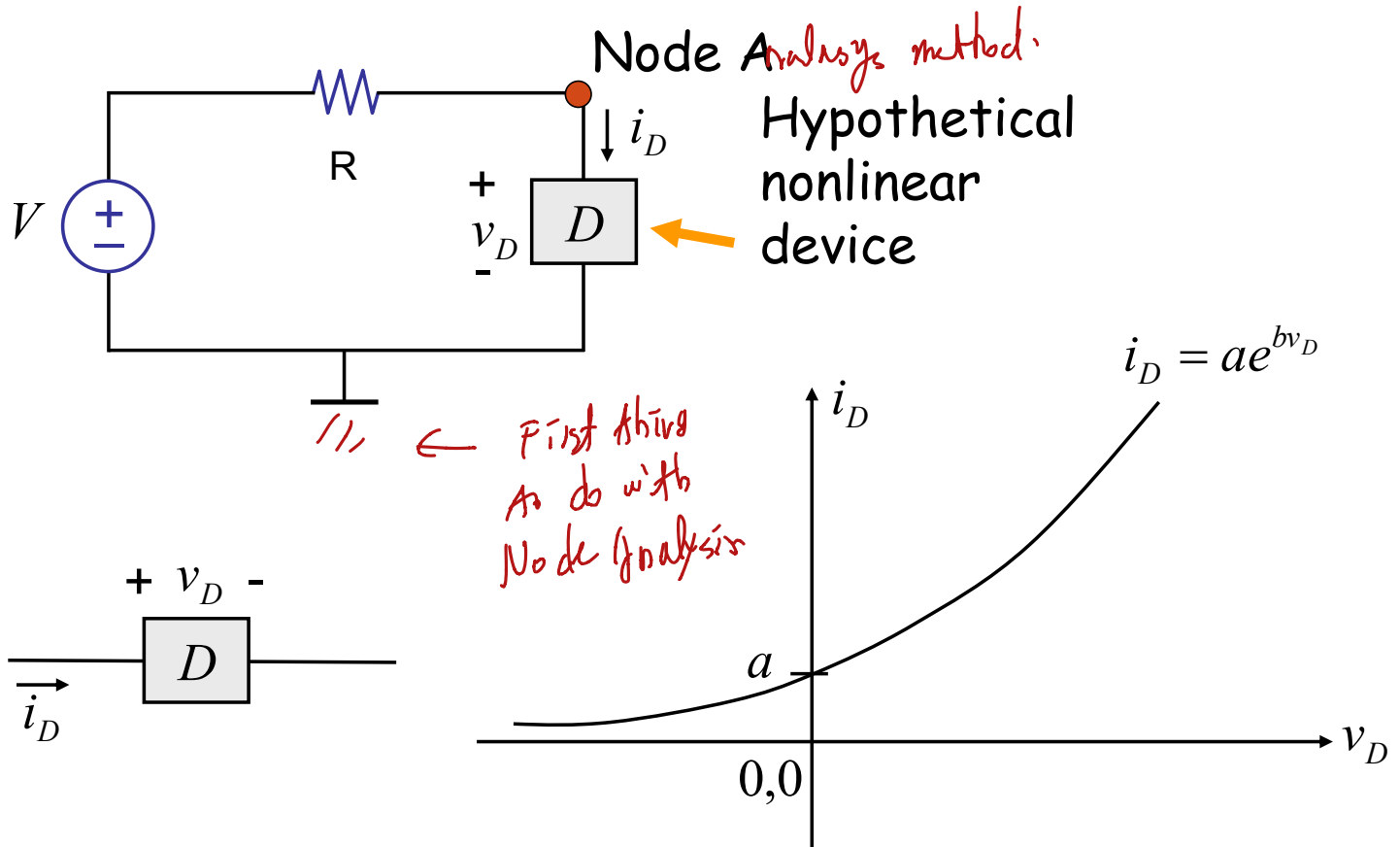

(Curiously, the device supplies power when v_D is negative)

Analytical Method

- Apply KCL at node A (the node method),

$$\frac{v_D - V}{R} + i_D = 0 \quad (1)$$

$$i_D = ae^{bv_D} \quad (2)$$

2 unknowns 2 equations


Solve the equation by

- trial and error
- numerical methods



Graphical Method

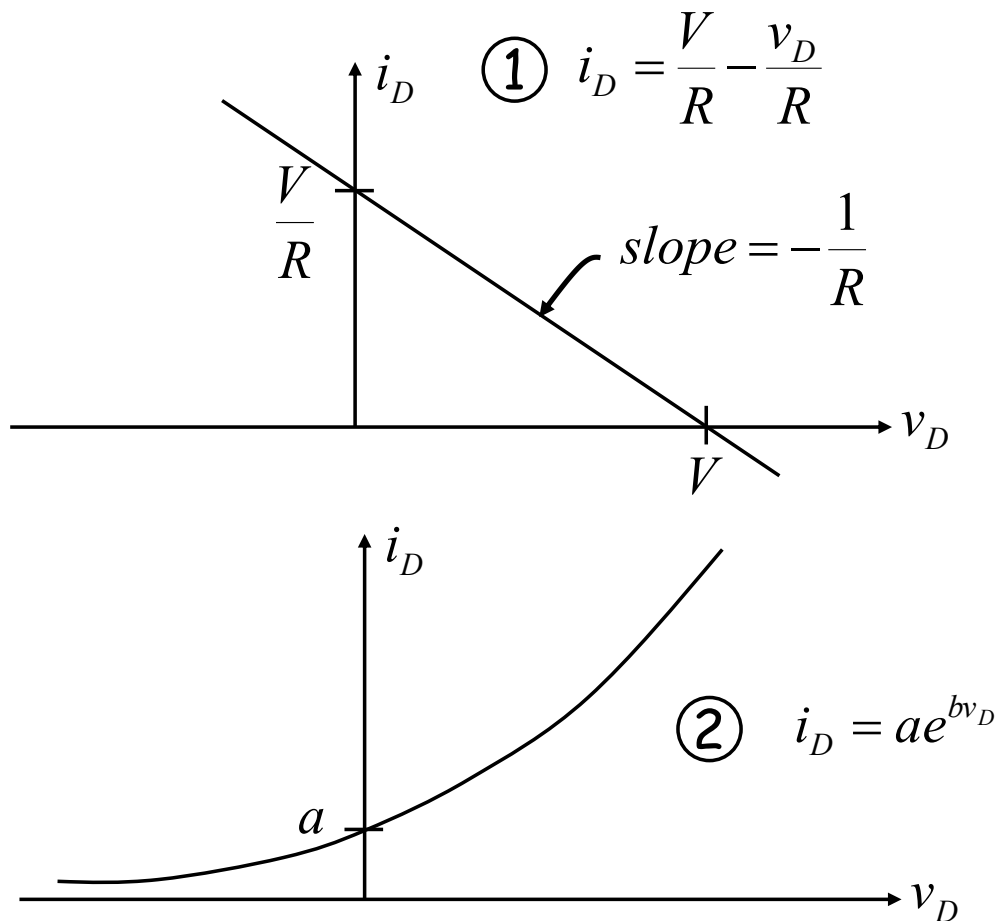
The solution should satisfy both equations



$$\frac{V_p - V}{R} + 0 = i_D$$

Graphical Method

Combine the two constraints

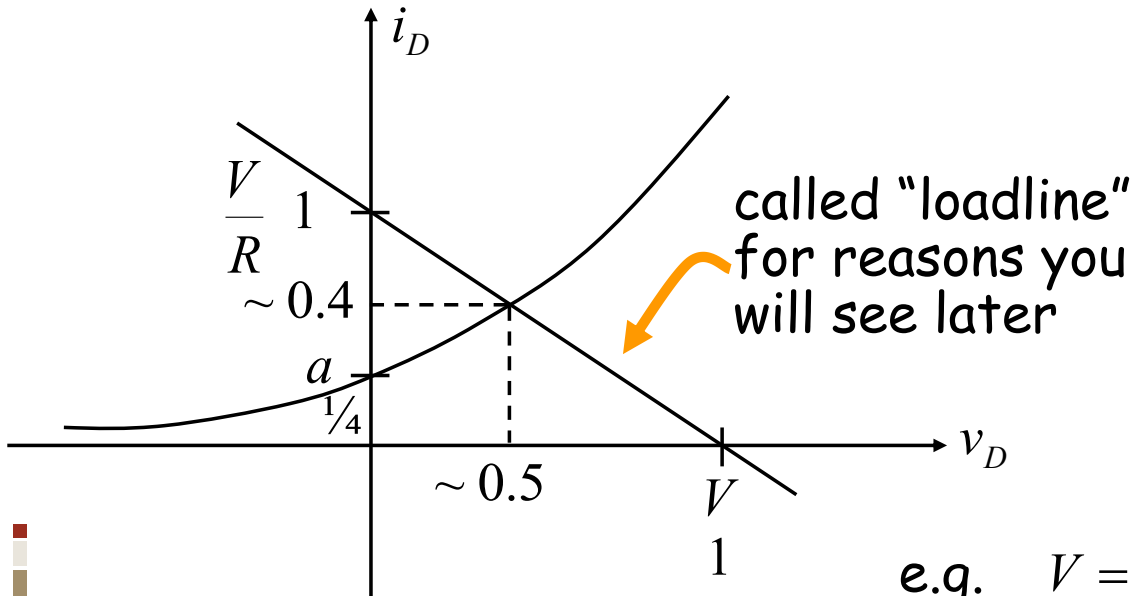

e.g. $V = 1$

$R = 1$

$a = \frac{1}{4}$




$b = 1$

$v_D = 0.5V$

$i_D = 0.4A$



Incremental Analysis

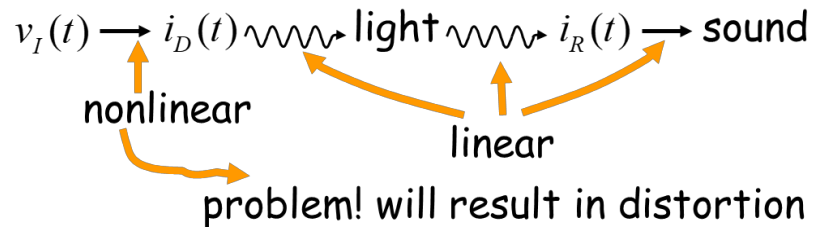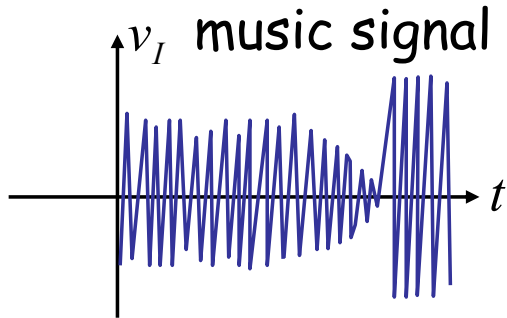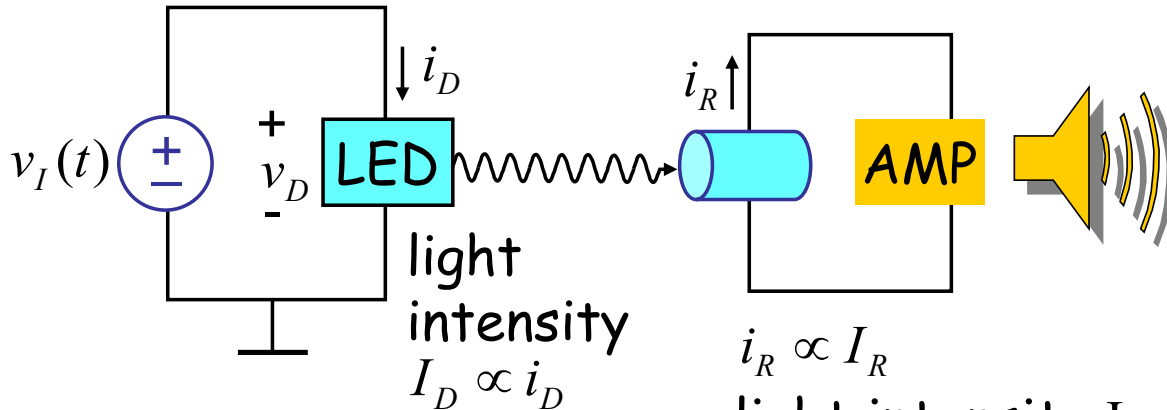- Assume our hypothetical LED is having $i_D = ae^{b \cdot v_D}$




Incremental Analysis

Non linear

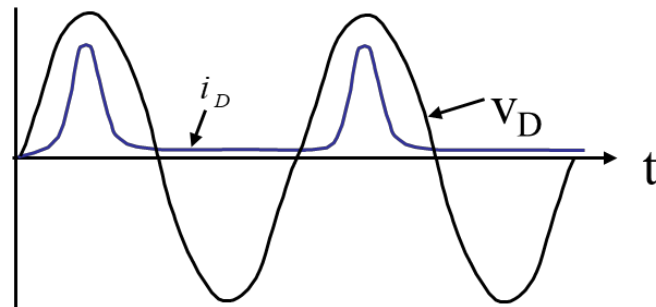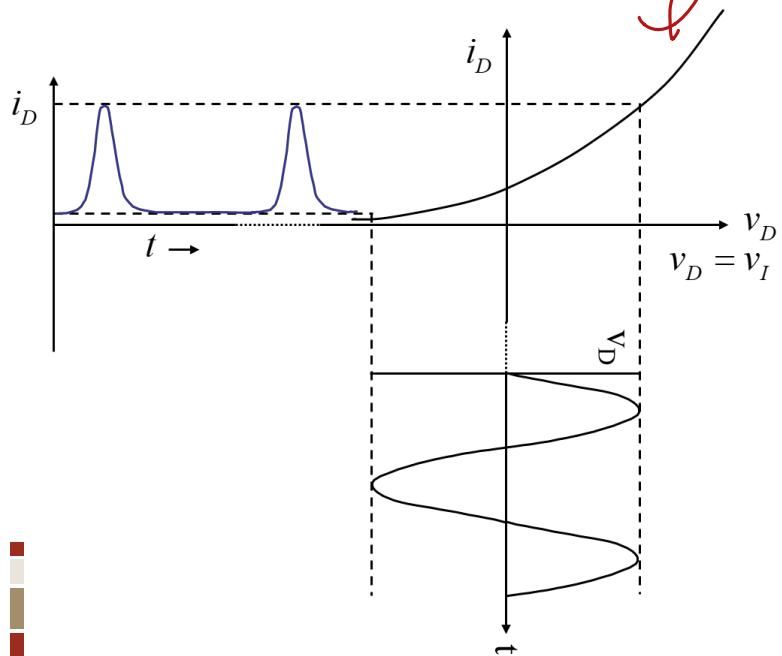


Incremental Analysis

- What we need is linear amplifier

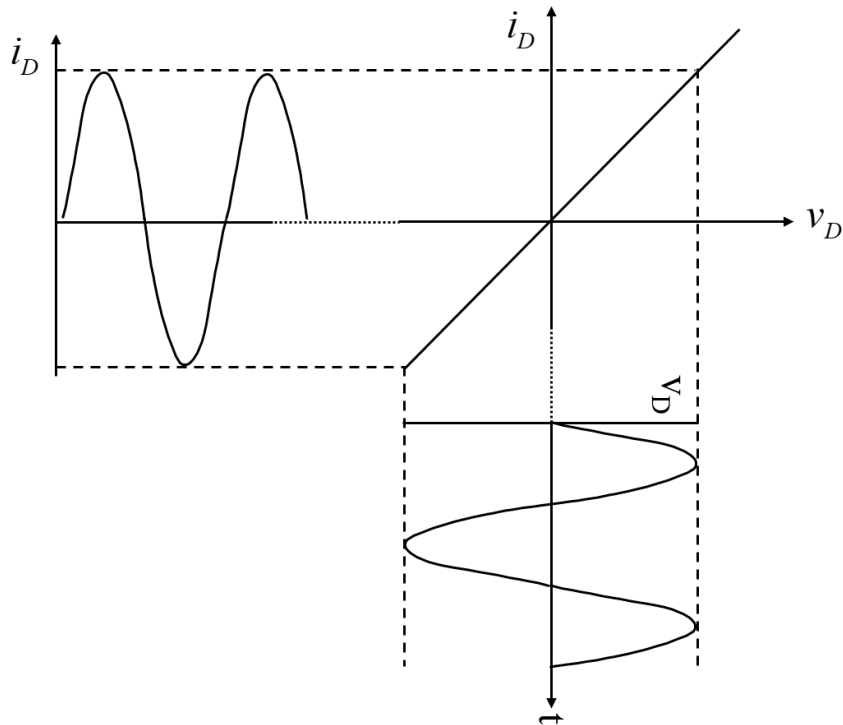


Linear amplifier from nonlinear element

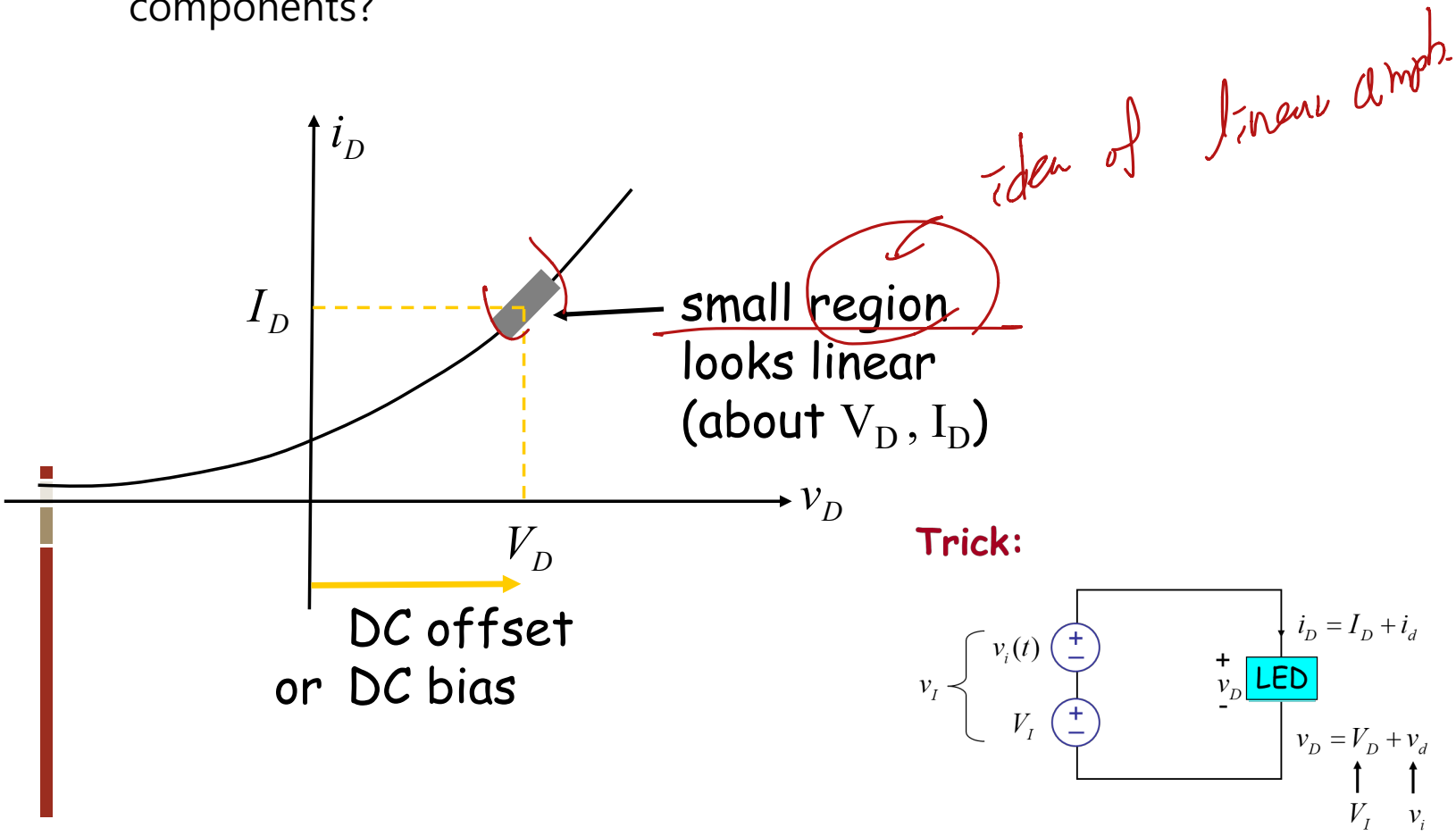- How can we implement linear amplifier from nonlinear components?





Result

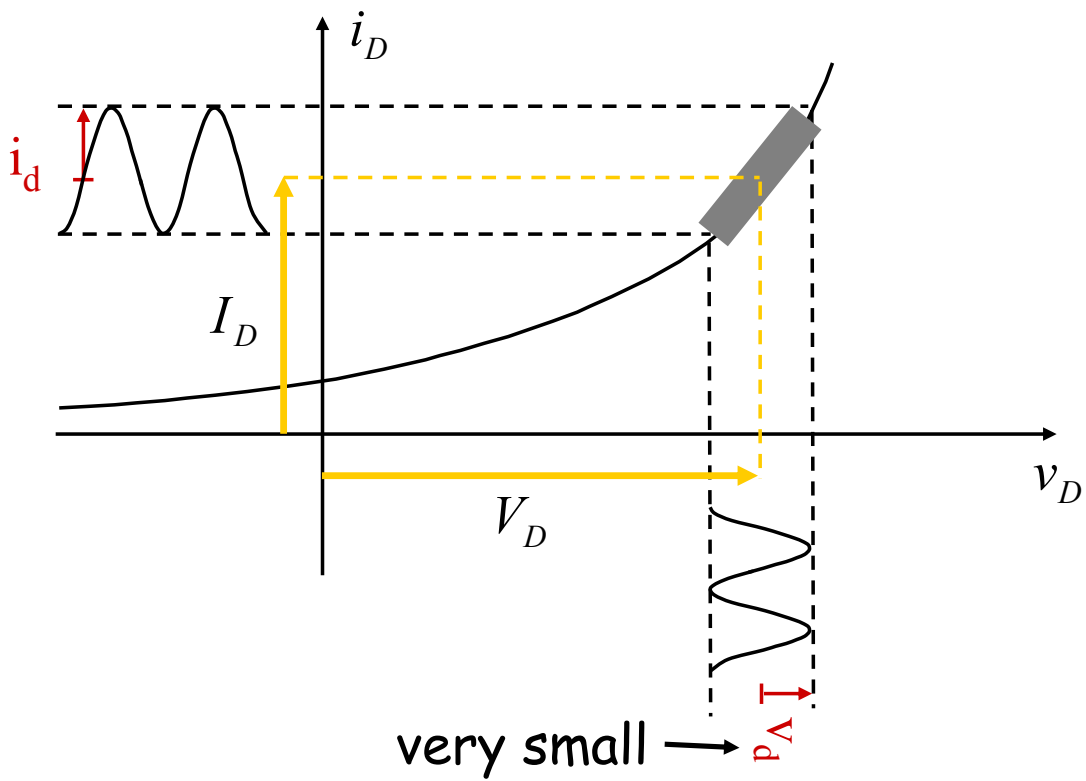




Result

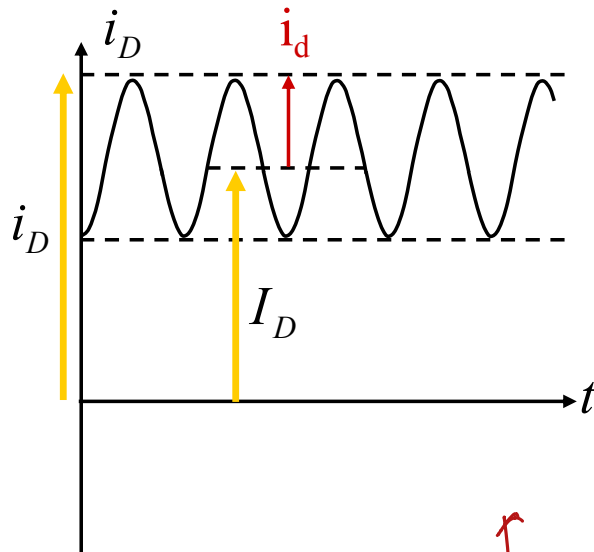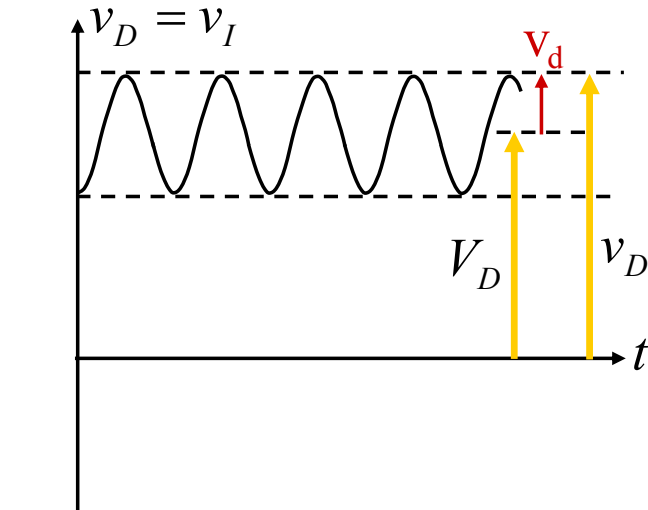

~linear!


add bias

because the problem is

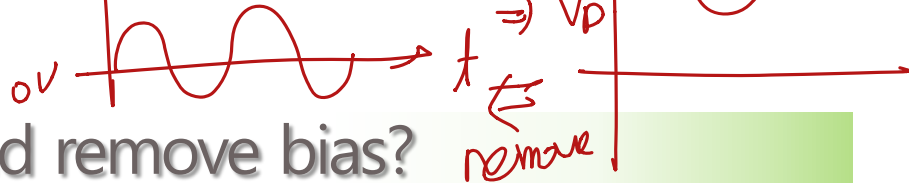


How can we apply and remove bias?

- How to add bias?

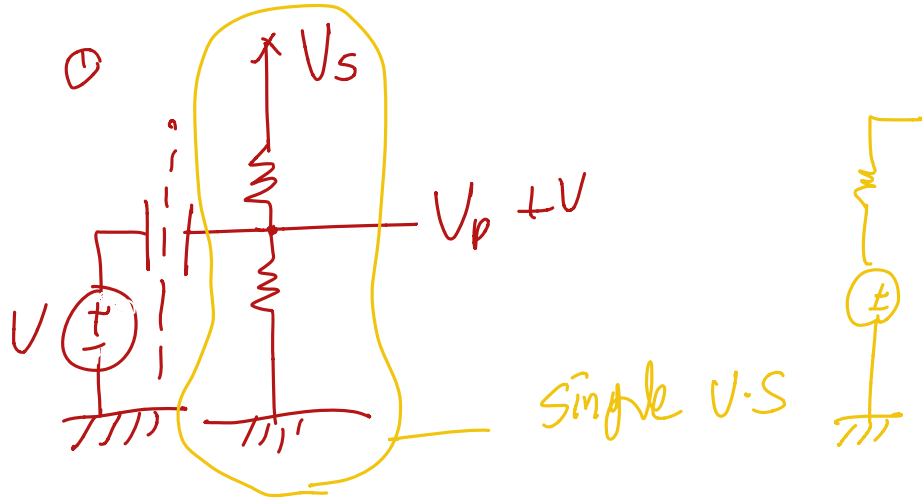

- How to remove bias?

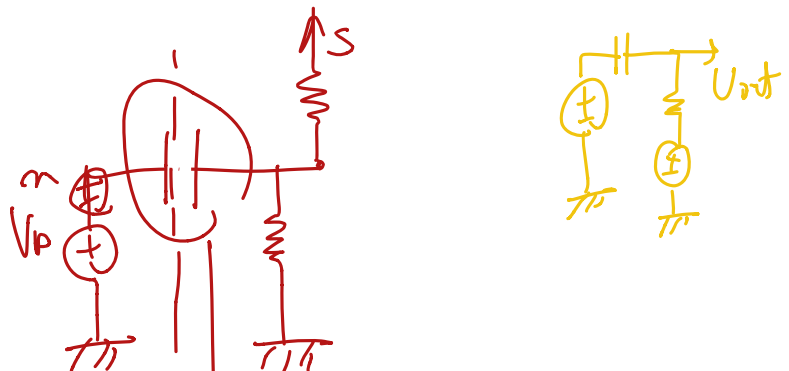

plugging in the values

Why is the small signal response linear?

- Can we guarantee that the response with respect to the small signal input always linear?

We replaced

$$i_D = f(v_D)$$

nonlinear

$$v_D = V_D + \Delta v_D$$

large DC b.i.m.
increment about V_D

$V_{b, v}$
→ DC bias @
combination of signal

using Taylor's Expansion to expand $f(v_D)$ near $v_D = V_D$:

$$i_D = f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D + \frac{1}{2!} \left. \frac{d^2 f(v_D)}{dv_D^2} \right|_{v_D=V_D} \cdot \Delta v_D^2 + \dots$$

neglect higher order terms because Δv_D is small

$$i_D \approx \underbrace{f(V_D)}_{\text{constant w.r.t. } \Delta v_D} + \underbrace{\left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D}}_{\text{constant w.r.t. } \Delta v_D, \text{ slope at } V_D, I_D} \cdot \Delta v_D$$

We can write

$$I_D + \Delta i_D \approx f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D$$

equating DC and time-varying parts,

$$I_D = f(V_D) \rightarrow \text{operating point}$$

$$\Delta i_D = \underbrace{\left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D}}_{\text{constant w.r.t. } \Delta v_D} \cdot \Delta v_D$$

$$\text{so, } \underline{D i_D \propto D v_D}$$

$$\begin{aligned} \text{By notation,} \\ D i_D &= i_d \\ D v_D &= v_d \end{aligned}$$

Example

$$i_D = a e^{b v_D}$$

$$I_D + i_d \approx a e^{b V_D} + a e^{b V_D} \cdot b \cdot v_d$$

Equate DC and incremental terms,

$$\boxed{I_D = a e^{b V_D}} \rightarrow \begin{array}{l} \text{operating point} \\ \text{[aka bias pt.} \\ \text{[aka DC offset} \end{array}$$


$$i_d = \underbrace{a e^{b V_D}}_{\text{constant}} b \cdot v_d$$

$$i_d = \underbrace{I_D \cdot b}_{\text{constant}} v_d \rightarrow \begin{array}{l} \text{small signal} \\ \text{behavior} \\ \rightarrow \text{linear!} \end{array}$$

Graphical Interpretation

$$I_D = a e^{bV_D} \rightarrow \text{operating point}$$


$$i_d = I_D \cdot b \cdot v_d$$

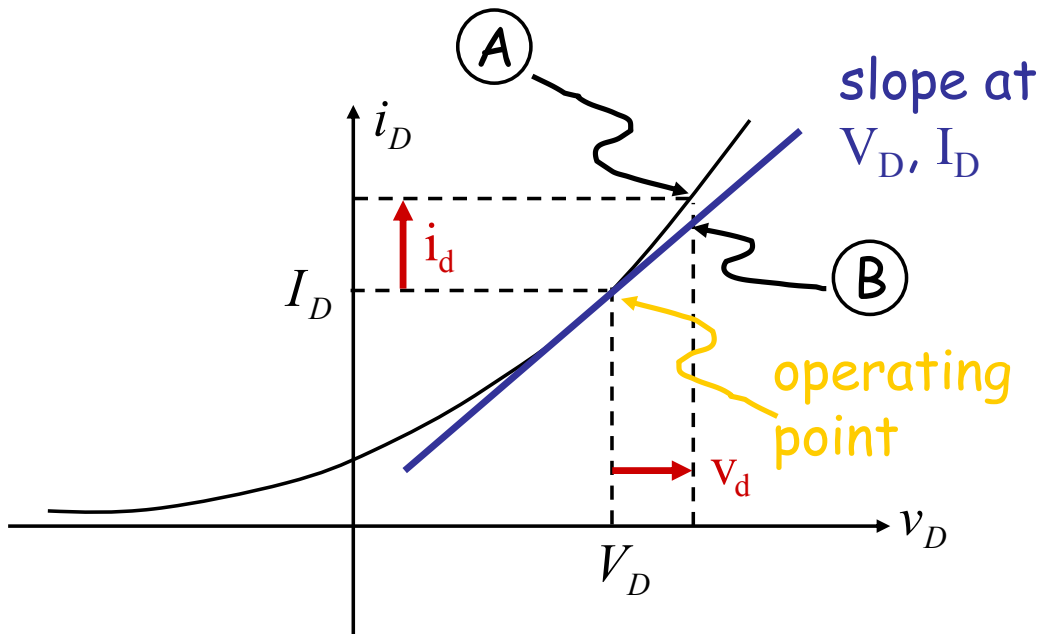

we are
approximating
(A) with (B)

Combined Together

Large signal circuit:

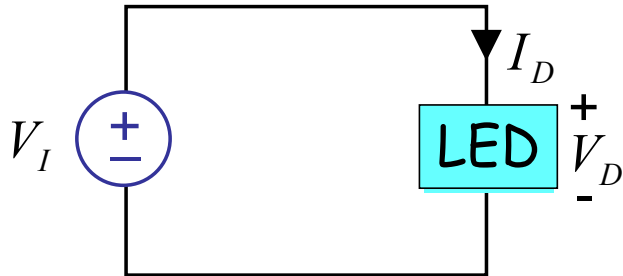


$$I_D = a e^{bV_D}$$

By using graphical or analytical solution, find bias point.


Small signal reponse: $i_d = I_D b v_d$

behaves like:

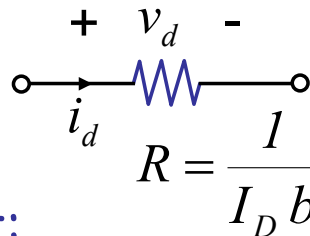

Linearization

small signal circuit:

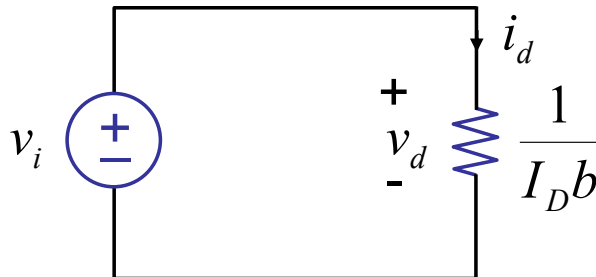

Linear!