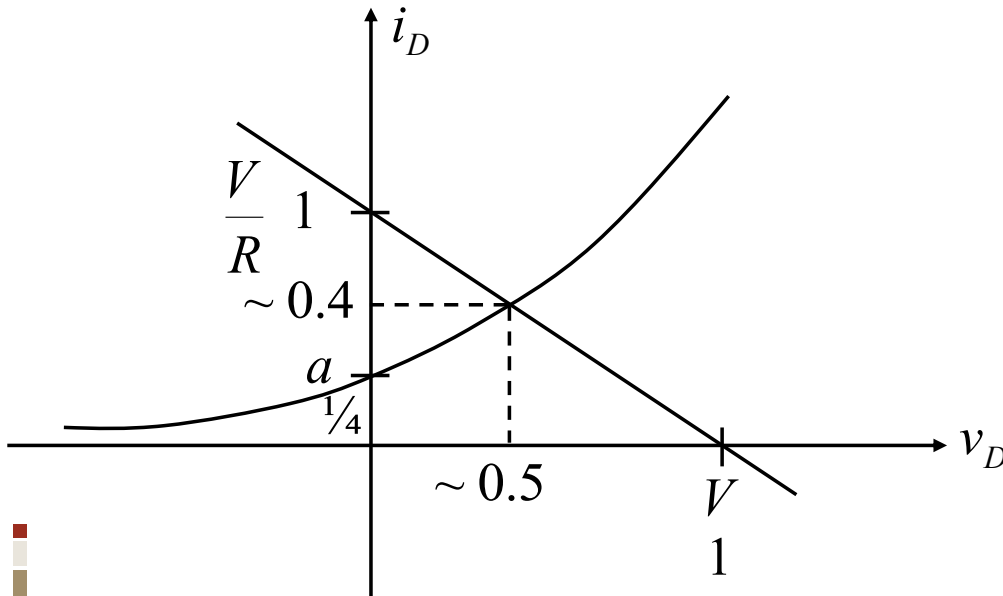


Numerical analysis

- In graphical method, we plotted the two constraints simultaneously.




e.g. $V = 1$ $v_D = 0.5V$
 $R = 1$ $i_D = 0.4A$
 $a = \frac{1}{4}$
 $b = 1$

- In numerical analysis, we should provide the two constraints in functional forms

Numerical analysis

- In numerical analysis, we should provide the two constraints in functional forms
 - Residuals of the eq1 ($i_D = \frac{V}{R} - \frac{v_D}{R}$): $i_D - (V - v_D)/R$
 - Residuals of the eq2 ($i_D = ae^{bv_D}$): $i_D - ae^{bv_D}$
 - We need to define a new function with the following input parameters and return values
 - Input: (v_D, i_D)
 - Output: Residues of (eq1, eq2) = $\left(i_D - \frac{V-v_D}{R}, i_D - ae^{bv_D}\right)$
 - Call `scipy.optimize.root("new function name", "list of initial guess for (v_D, i_D) ")`
 - By using the numerical analysis, we can find the correct value should be $v_D = 0.562V$ and $i_D = 0.438A$.
 - Check "Finding numerical solution.ipynb"


Incremental Analysis

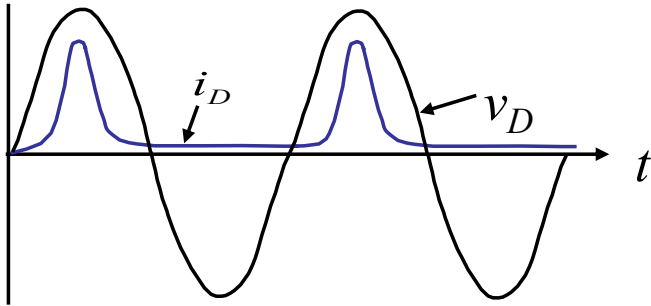


- Demonstration of sound and signal distortion
 - Monotone.ipynb
 - Record sound.ipynb

Linear amplifier from nonlinear element

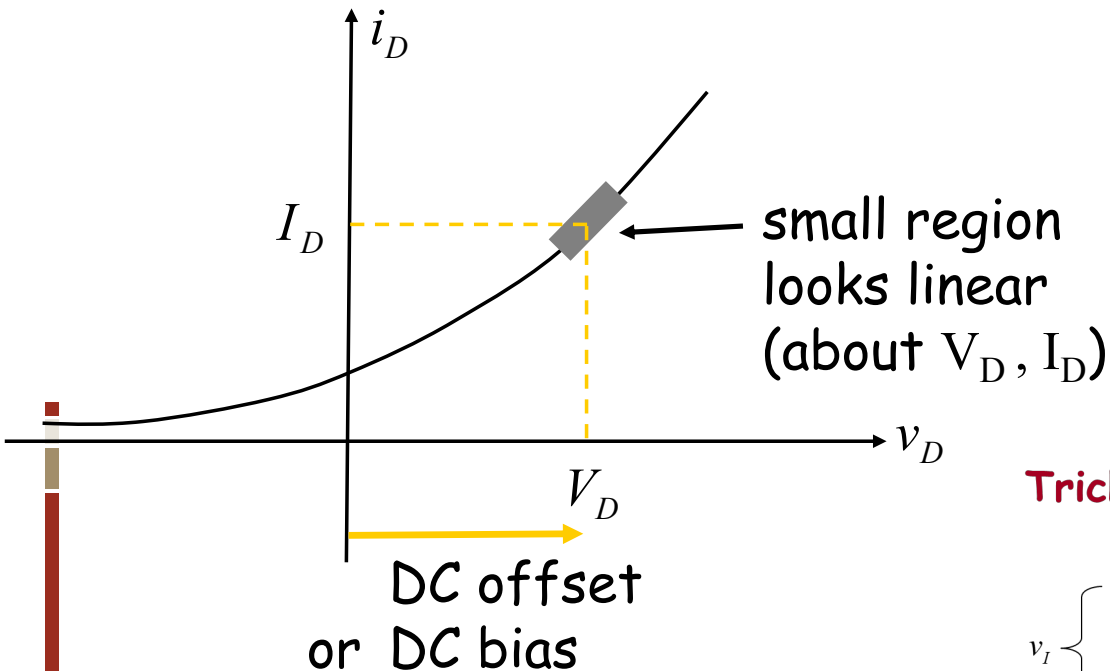
- How can we implement linear amplifier from nonlinear components?



Trick:

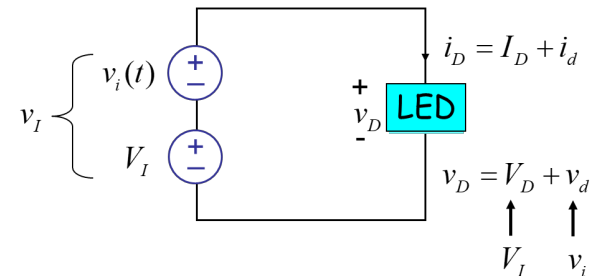

Result

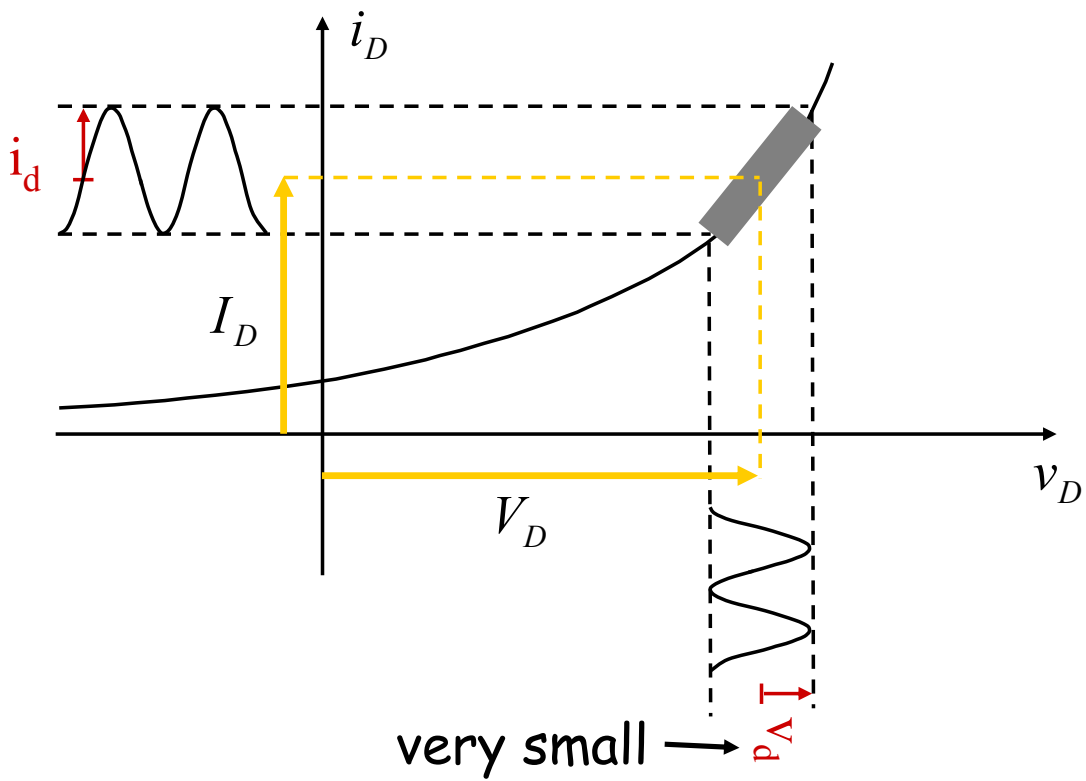



Taylor expansion

- Assume that we are given some arbitrary function $f(x)$ of x .
-
- Question: can we approximate this function as a some of polynomials of x ?
In other words,

$$f(x) = c_0 + c_1x + c_2x^2 + c_3x^3 + \dots$$

- Answer: it depends on the types of function, but for many of the functions, it is possible.
-
- Question: the how can we find out $c_0, c_1, c_2, c_3, \dots$?
- Answer: by matching the values of the derivatives at $x = x_0$.
- In general, $f(x) = f(x_0) + \frac{df}{dx}\bigg|_{x=x_0} (x - x_0) + \frac{1}{2!} \frac{d^2f}{dx^2}\bigg|_{x=x_0} (x - x_0)^2 + \frac{1}{3!} \frac{d^3f}{dx^3}\bigg|_{x=x_0} (x - x_0)^3 + \dots$
- Example 1) at $x = 0$, $f(x) = 1 + 2x + 3x^3 = c_0 + c_1x + c_2x^2 + c_3x^3 + \dots$
- Example 2) at $x = 1$, $f(x) = 1 + 2x + 3x^3 = c_0 + c_1(x - 1) + c_2(x - 1)^2 + c_3(x - 1)^3 + \dots$

Why is the small signal response linear?

- Can we guarantee that the response with respect to the small signal input always linear?

$$i_D = f(v_D)$$

nonlinear

We replaced

$$v_D = V_D + \Delta v_D$$

large DC

increment about V_D

using Taylor's Expansion to expand $f(v_D)$ near $v_D = V_D$:

$$i_D = f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D + \frac{1}{2!} \left. \frac{d^2 f(v_D)}{dv_D^2} \right|_{v_D=V_D} \cdot \Delta v_D^2 + \dots$$

neglect higher order terms because Δv_D is small

$$i_D \approx \underbrace{f(V_D)}_{\text{constant w.r.t. } \Delta v_D} + \underbrace{\left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D}}_{\text{constant w.r.t. } \Delta v_D, \text{ slope at } V_D, I_D} \cdot \Delta v_D$$

We can write

$$I_D + \Delta i_D \approx f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D$$

equating DC and time-varying parts,

$$I_D = f(V_D) \rightarrow \text{operating point}$$

$$\Delta i_D = \underbrace{\left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D}}_{\text{constant w.r.t. } \Delta v_D} \cdot \Delta v_D$$

$$\text{so, } \Delta i_D \propto \Delta v_D$$

By notation,

$$\Delta i_D = i_d$$

$$\Delta v_D = v_d$$



Incremental Method (Small Signal Method)

1. Operate at some DC offset or bias point V_D, I_D .
2. Superimpose small signal v_d (music) on top of V_D .
3. Response i_d to small signal v_d is approximately linear.

Notation: $i_D = I_D + i_d$

total
variable

DC
offset

small
superimposed
signal

Example

$$i_D = a e^{b v_D}$$

$$I_D + i_d \approx a e^{b V_D} + a e^{b V_D} \cdot b \cdot v_d$$

Equate DC and incremental terms,

$$\boxed{I_D = a e^{b V_D}} \rightarrow \begin{array}{l} \text{operating point} \\ \text{[aka bias pt.} \\ \text{[aka DC offset} \end{array}$$


$$i_d = \underbrace{a e^{b V_D}}_{\text{constant}} b \cdot v_d$$

$$i_d = \underbrace{I_D \cdot b}_{\text{constant}} v_d \rightarrow \begin{array}{l} \text{small signal} \\ \text{behavior} \\ \rightarrow \text{linear!} \end{array}$$

Graphical Interpretation

$$I_D = a e^{bV_D} \rightarrow \text{operating point}$$


$$i_d = I_D \cdot b \cdot v_d$$

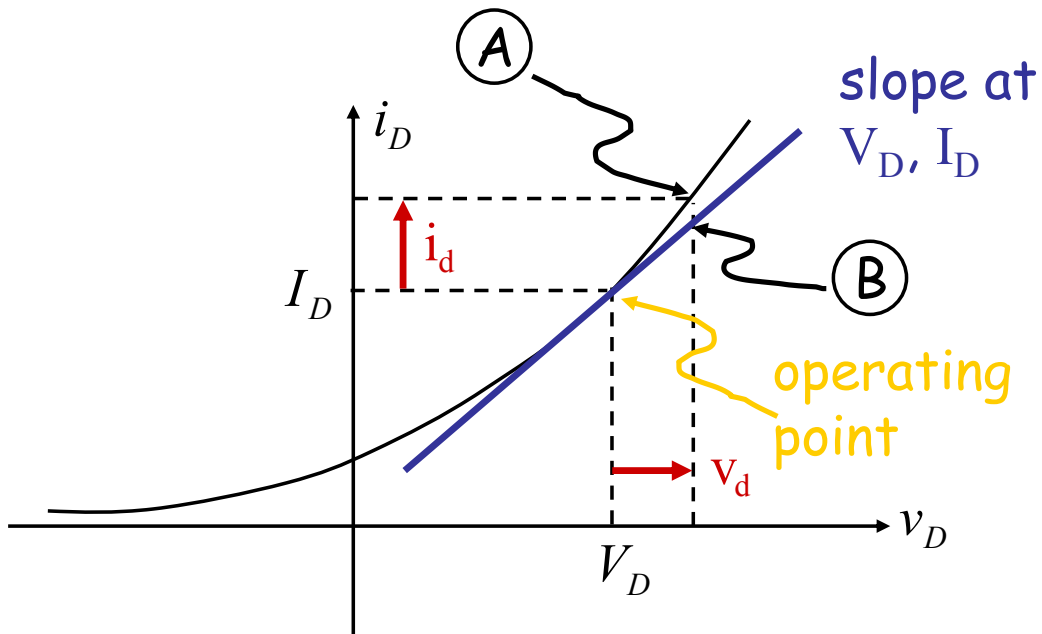

we are
approximating
Ⓐ with Ⓑ

Combined Together

Large signal circuit:

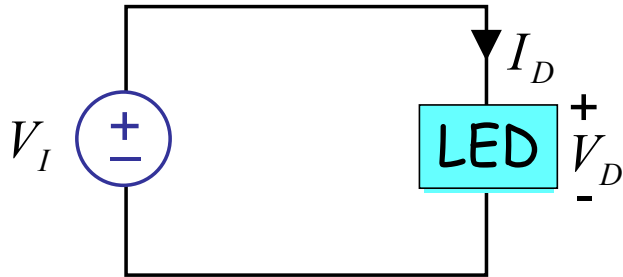


$$I_D = a e^{bV_D}$$

By using graphical or analytical solution, find bias point.


Small signal reponse: $i_d = I_D b v_d$

behaves like:

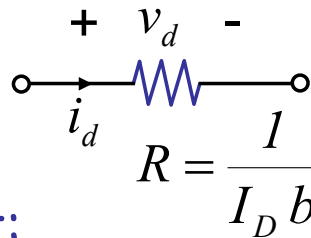

Linearization


small signal circuit:

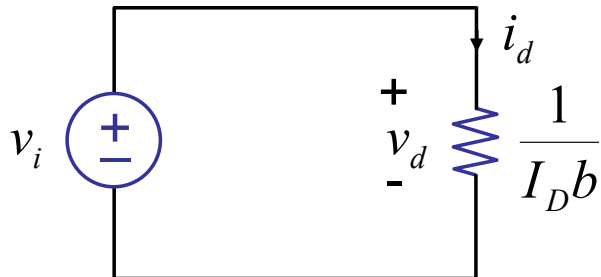

Linear!


Piecewise Linear Analysis

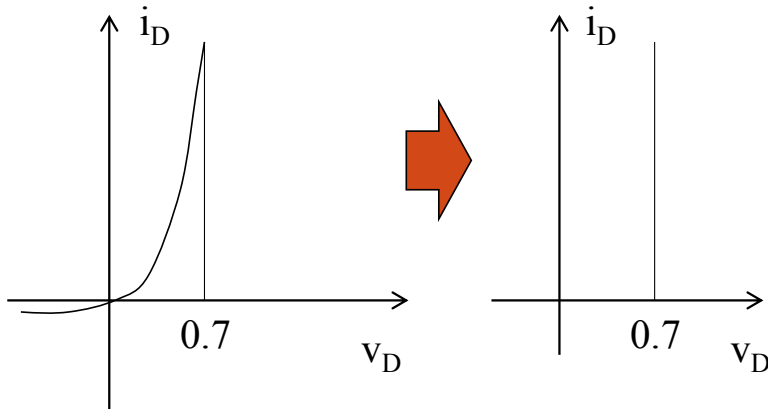- Diode: $i_D = I_s(e^{v_D/V_{TH}} - 1)$
- Analyze the circuit in two regimes



Open circuit case

- When $v_D < 0.7$ V

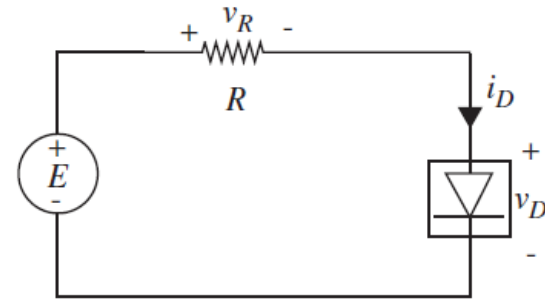


Close circuit case

- When $v_D > 0.7$ V

Dependent sources

- Section 2.6 in the textbook

New type of device: Dependent source

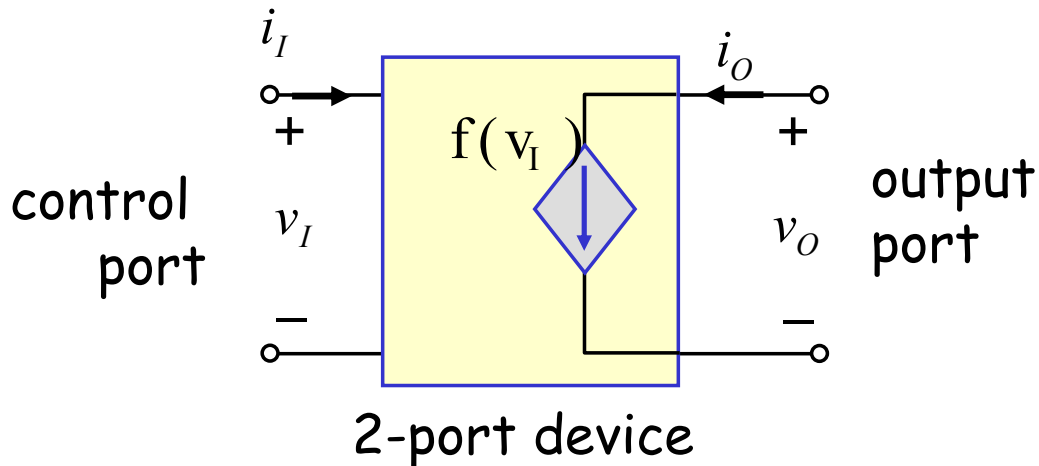


E.g., Voltage Controlled Current Source
Current at output port is a function of voltage at the input port

Independent Source Example

Example 1: Find V




independent
current
source

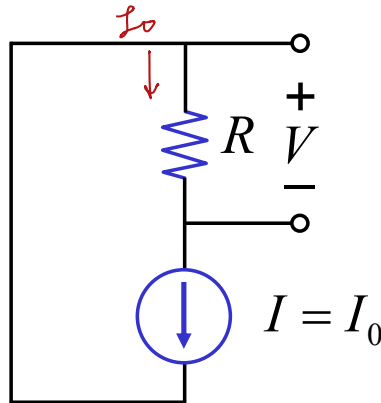

$$V = I_0 R$$

Dependent sources: Example


voltage
controlled
current
source

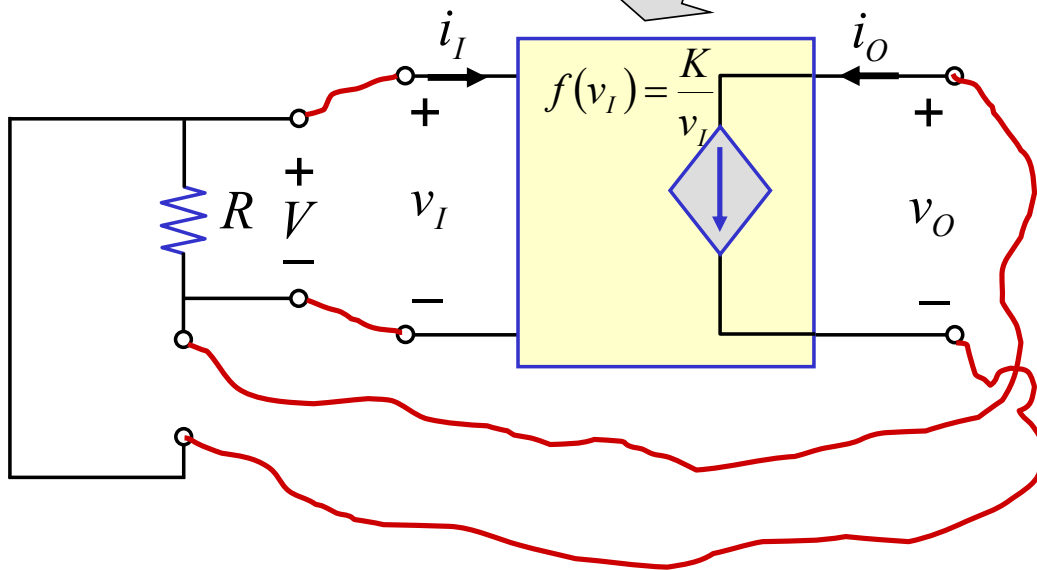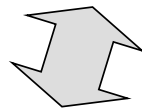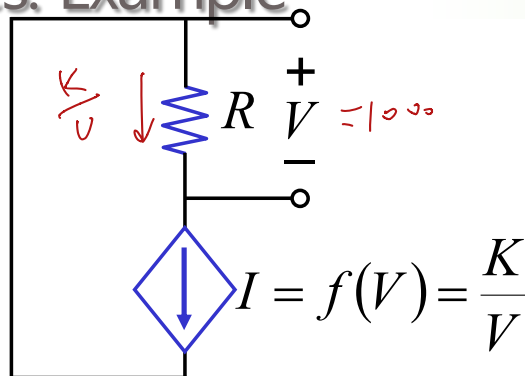

Dependent sources: Example

- Find V

voltage
controlled
current
source

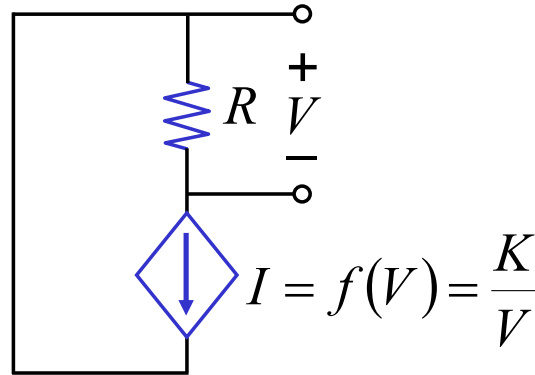

e.g. $K = 10^{-3} \text{ Amp} \cdot \text{Volt}$
 $R = 1\text{k}\Omega$

$$V = IR = \frac{K}{V} R$$

or $V^2 = KR$

or $V = \sqrt{KR}$
 $= \sqrt{10^{-3} \cdot 10^3}$
 $= 1 \text{ Volt}$

Another Dependent Source Example


- Assume there exists a hypothetical voltage-controlled current source

$$i_D = f(v_{IN})$$

e.g. $i_D = f(v_{IN})$

$$= \frac{K}{2} (v_{IN} - 1)^2 \quad \text{for } v_{IN} \geq 1$$

$$i_D = 0 \quad \text{otherwise}$$

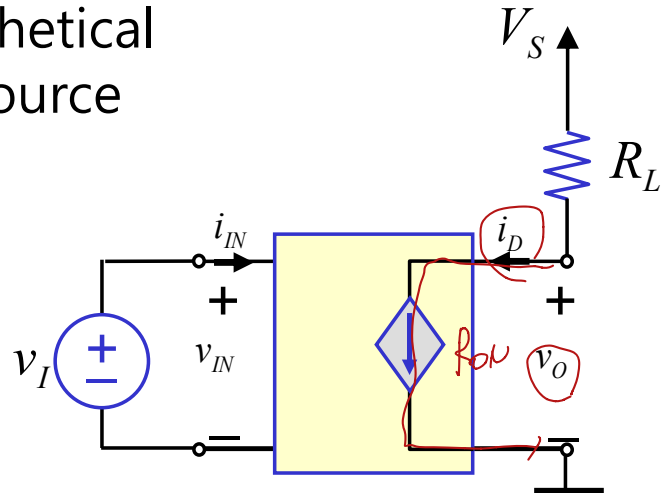


Find v_O as a function of v_I .

$$\approx i_D \cdot R_{OL}$$



Amplifier

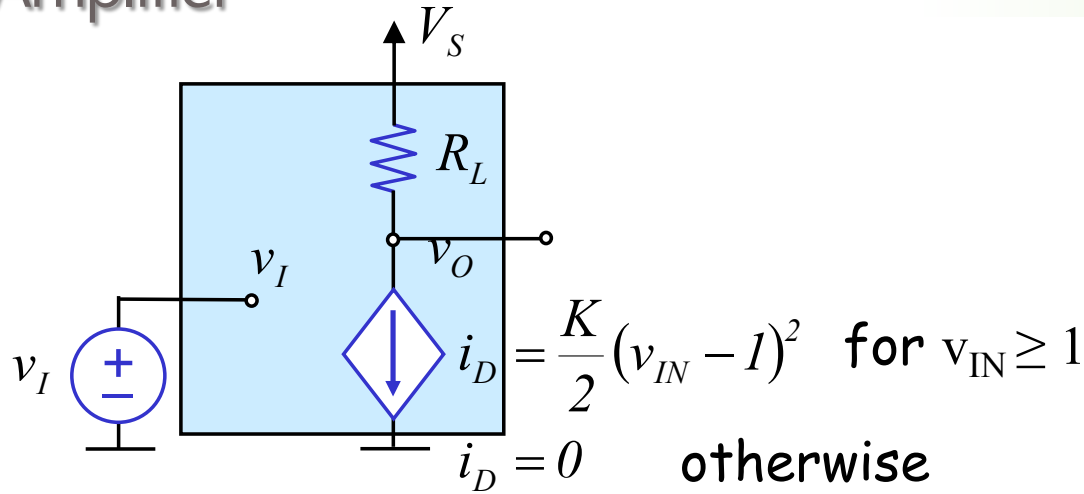

$$v_O = V_S - \frac{K}{2} (v_I - 1)^2 R_L \quad \text{for } v_I \geq 1$$

$$v_O = V_S \quad \text{for } v_I < 1$$






What is the gain of this amplifier?

Let's look at the v_O versus v_I curve.

e.g. $V_S = 10V$, $K = 2 \frac{mA}{V^2}$, $R_L = 5k\Omega$

$$v_O = V_S - \frac{K}{2} R_L (v_I - 1)^2$$

$$v_O = 10 - 5(v_I - 1)^2$$

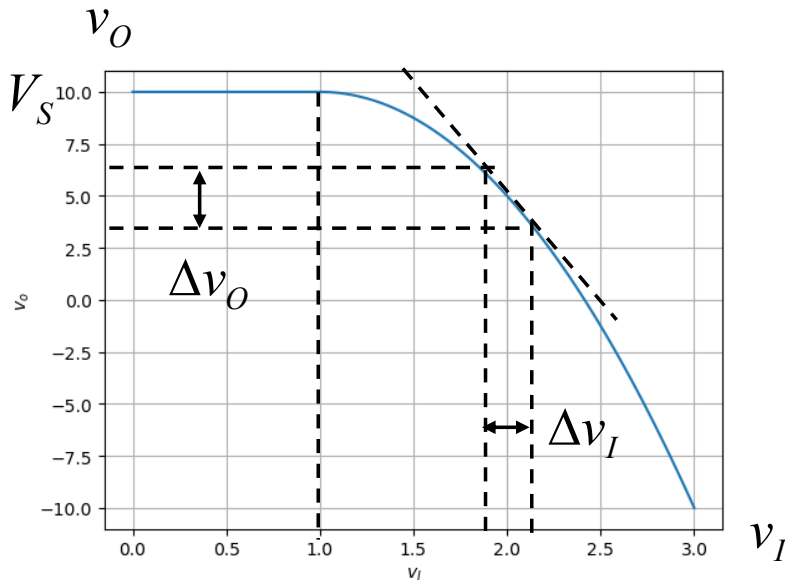


$$\frac{\Delta v_O}{\Delta v_I} > 1 \rightarrow \text{amplification}$$

$$\text{Amplification } \frac{\Delta v_O}{\Delta v_I} = -10$$


around $v_I = 2V$.




Other Types of Controlled Sources

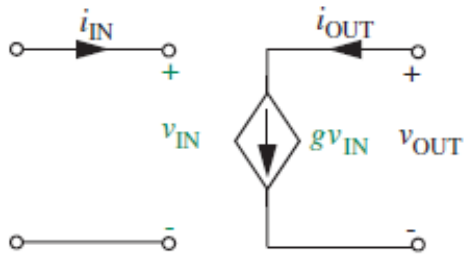


VCCS (voltage-controlled current source)

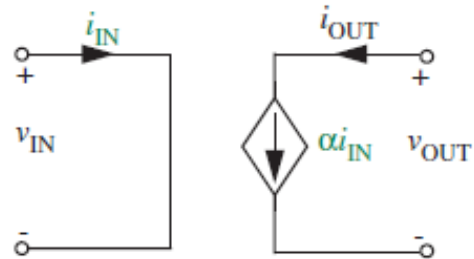

CCCS (current-controlled current source)

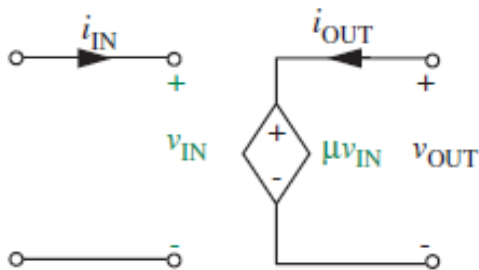

VCVS (voltage-controlled voltage source)

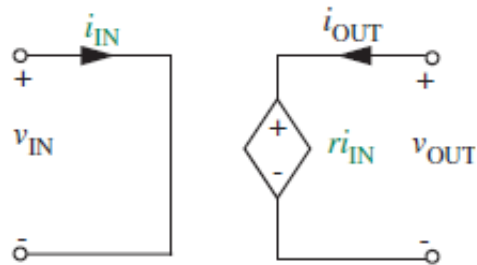

CCVS (current-controlled voltage source)

